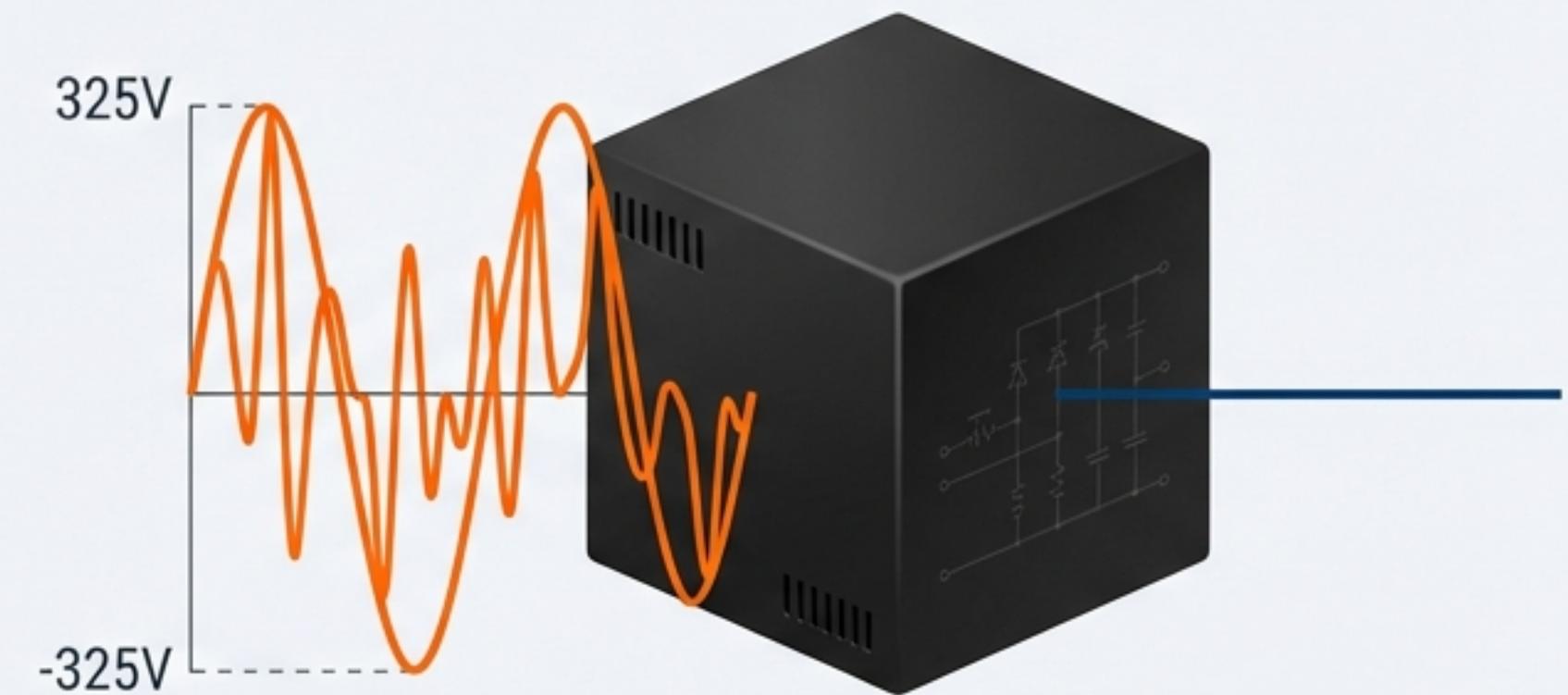


Rectification & Power Supplies


Unit 12 | Phase 2
Electrical Instrumentation



$$V_{DC} = \frac{2V_p}{\pi}$$


The Raw Material vs. The Requirement

AC: Alternating Current

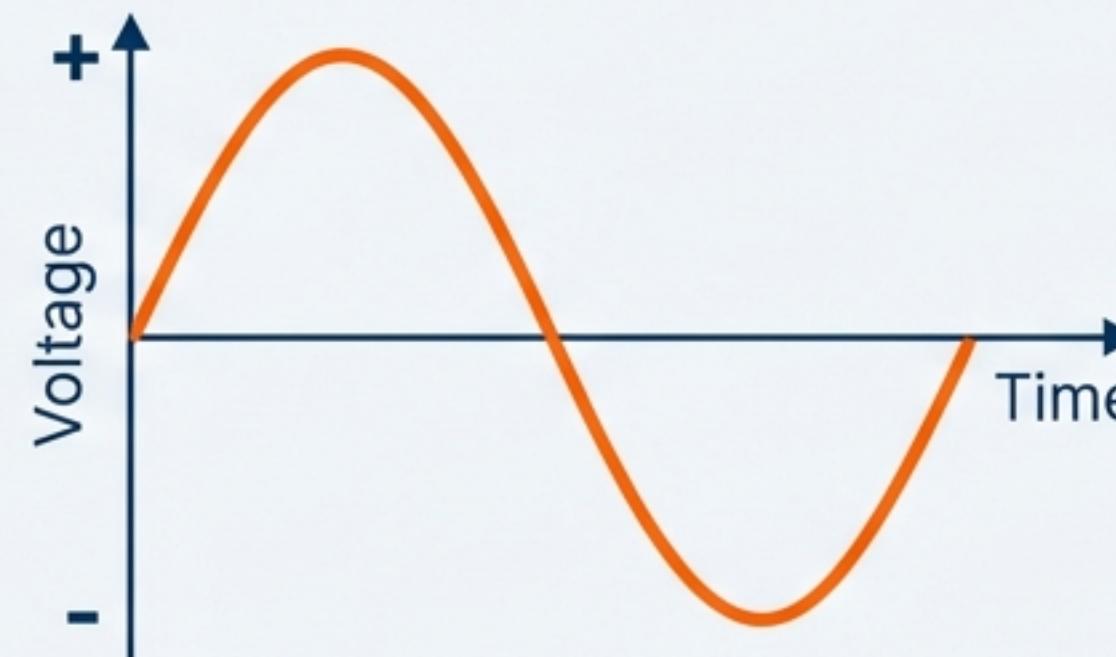

Rectification

DC: Direct Current

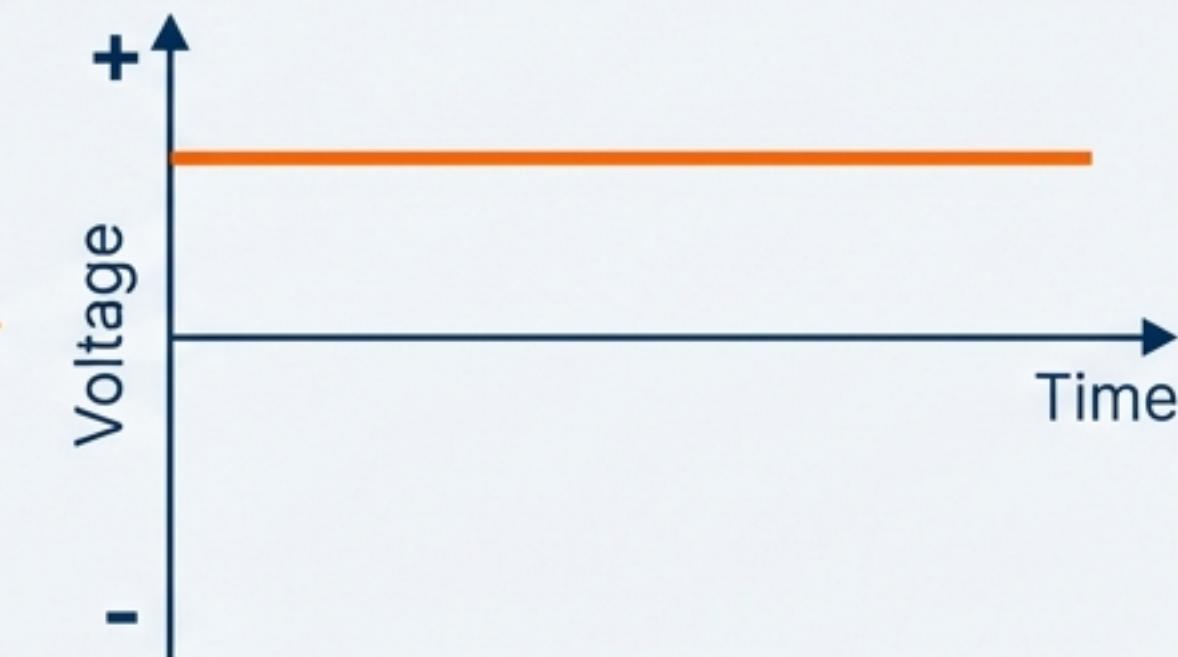


- Source: Mains Supply (ESB)
- 230V RMS, 50Hz
- Efficient for transmission


- Source: Batteries/Power Supplies
- One-way constant flow
- Required for Microchips & PLCs

The Gatekeeper: The Semiconductor Diode

Water Allowed Pass

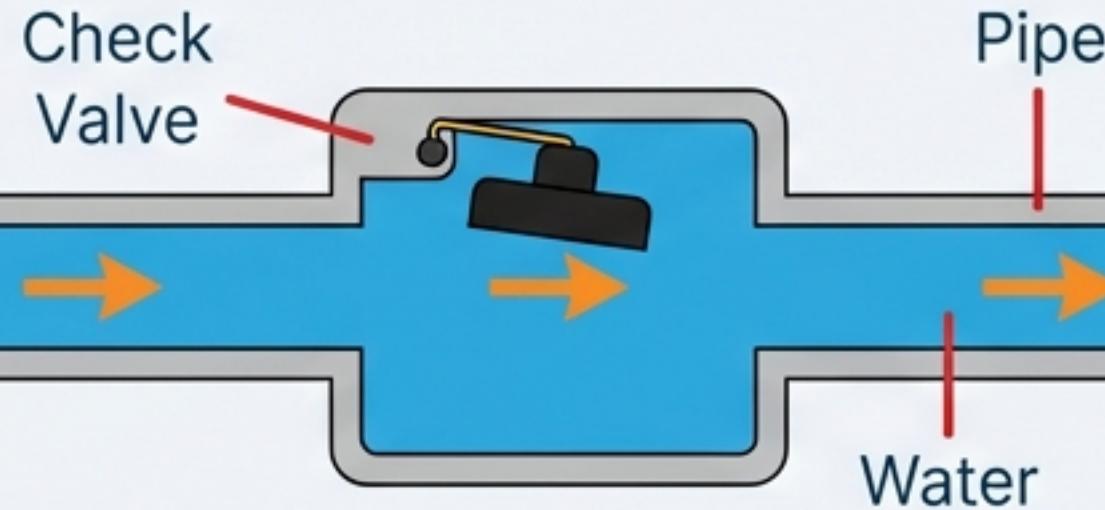

Water Not Allowed Pass

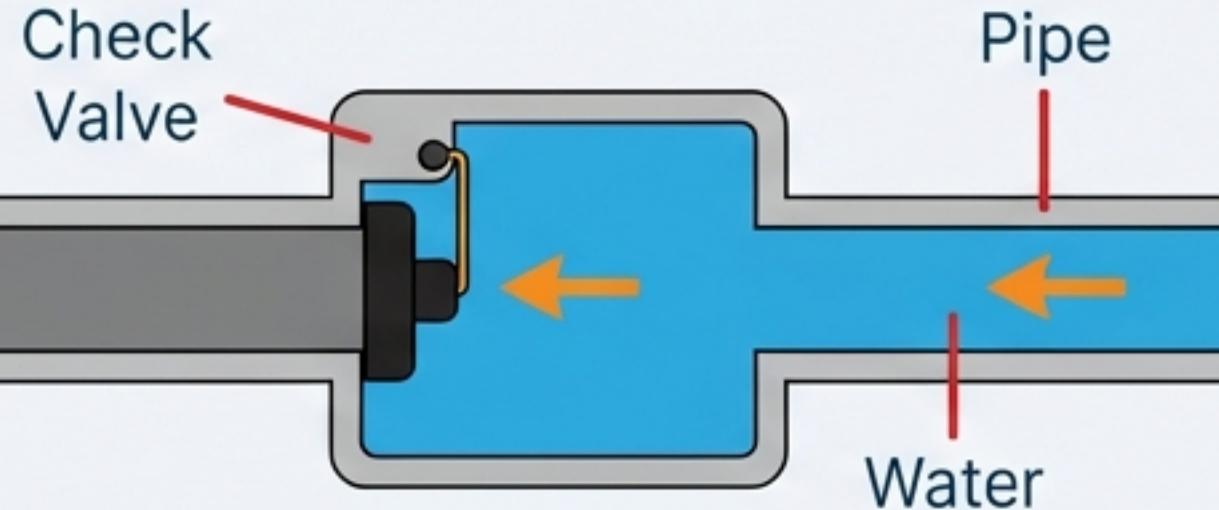


1. Forward Bias (Switch Closed):

Current flows.
Cost ~0.6V.


2. Reverse Bias (Switch Open):

Current blocked.

Current Flow

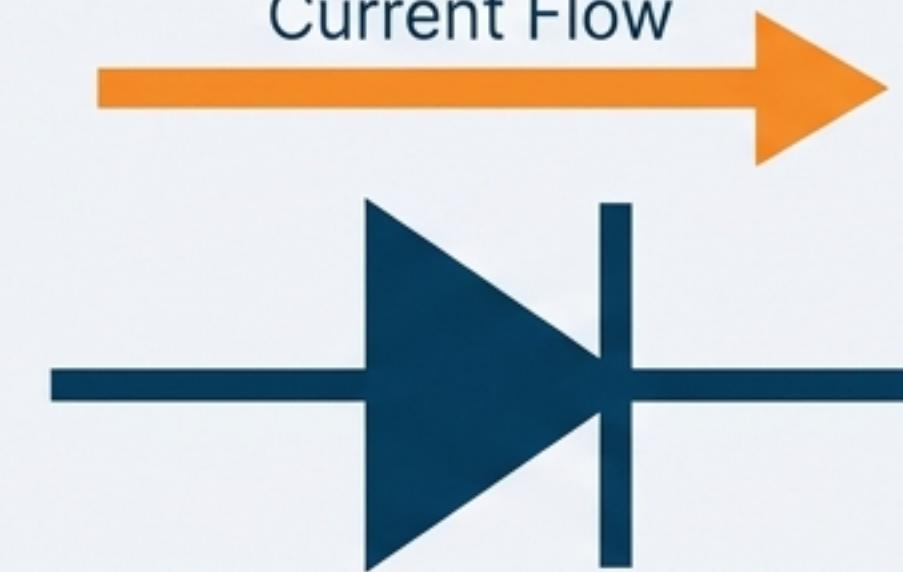

Stepping Down the Voltage

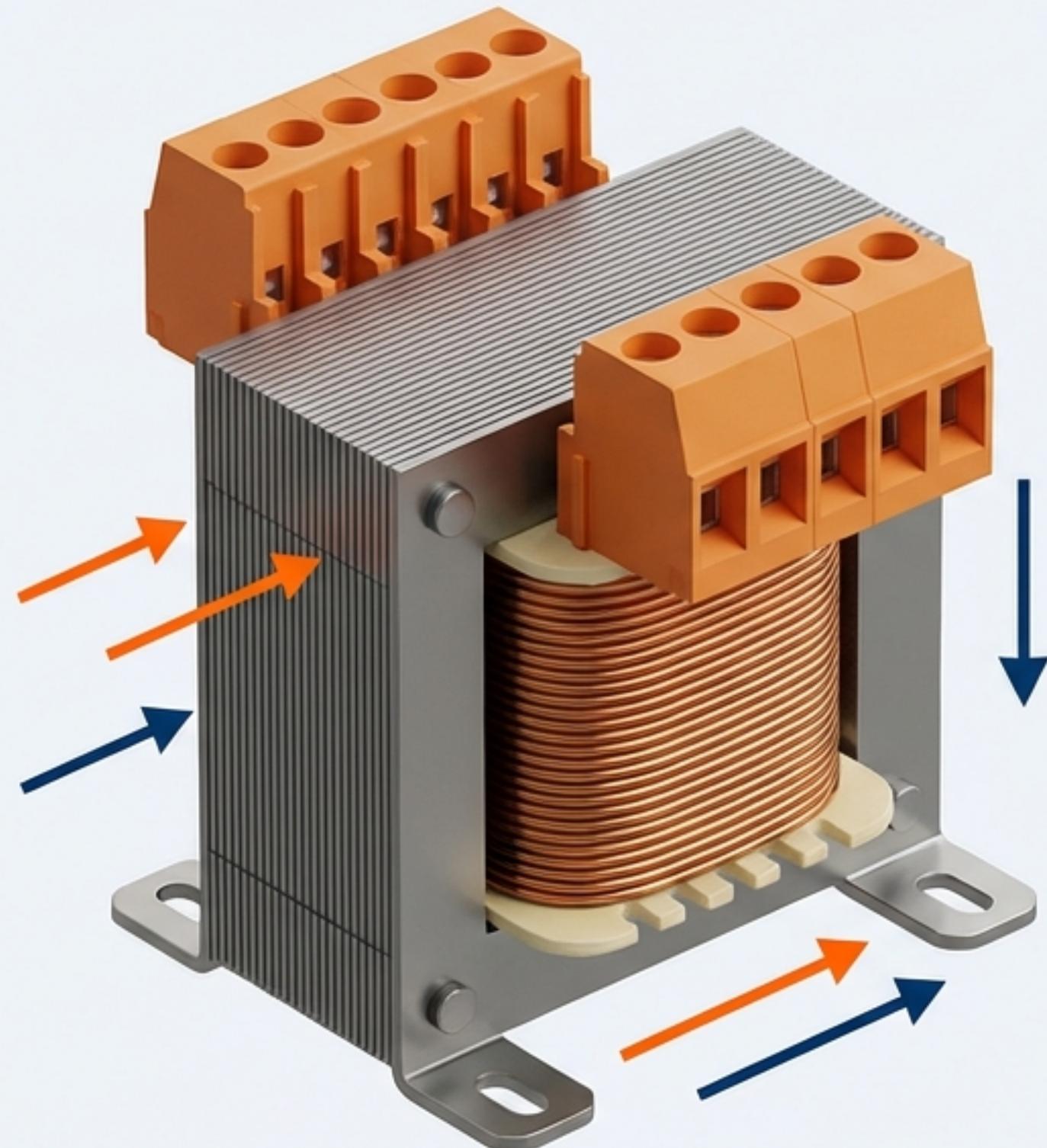

Key Principles



- **Mutual Inductance:** Voltage transfer via magnetic field (AC Only).
- **Isolation:** No electrical connection between Mains and Output.

$$\frac{V_p}{V_s} = \frac{N_p}{N_s}$$

Example:

Example: 10:1 Ratio on 240V Input = 24V Output.




First Attempt: Half-Wave Rectification

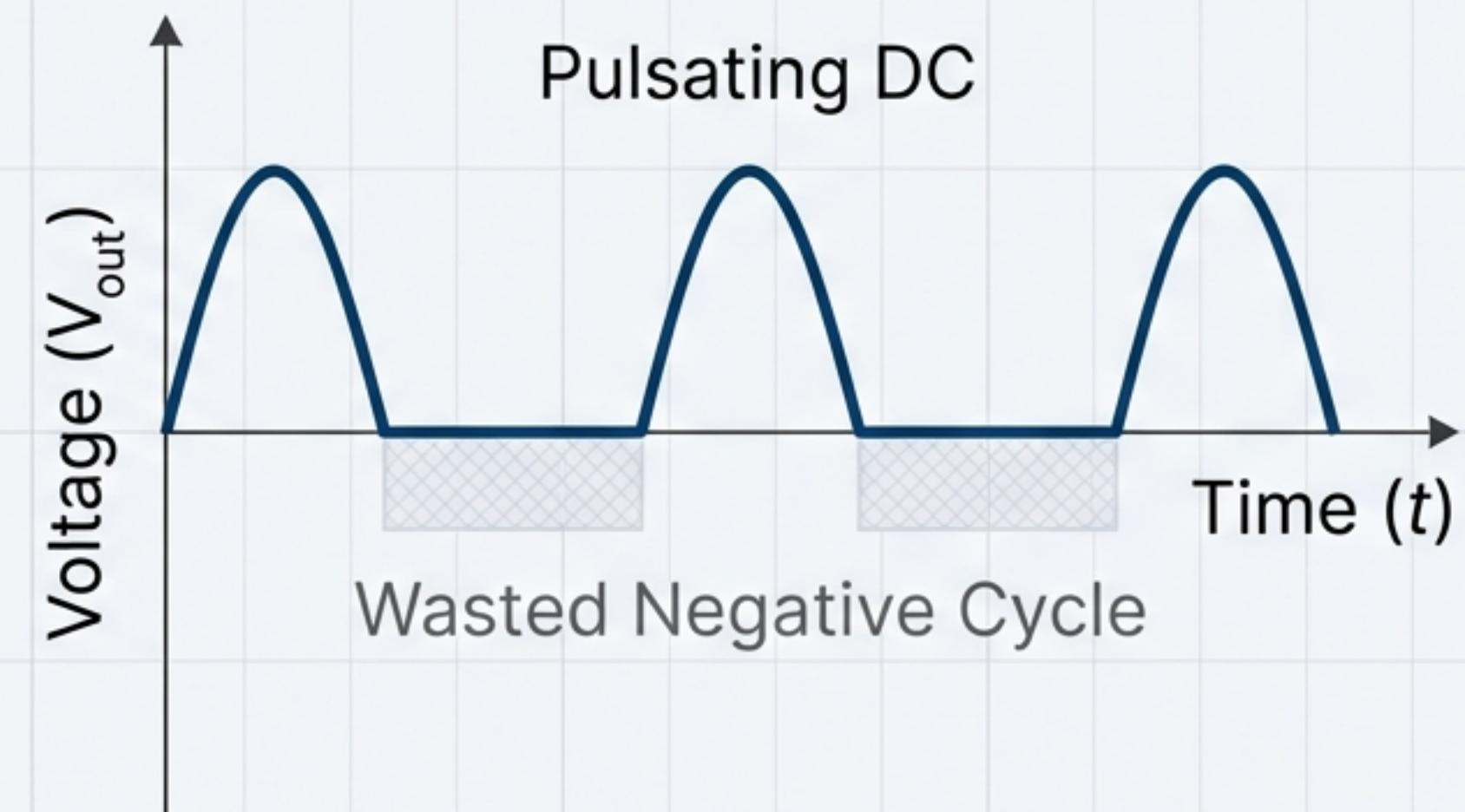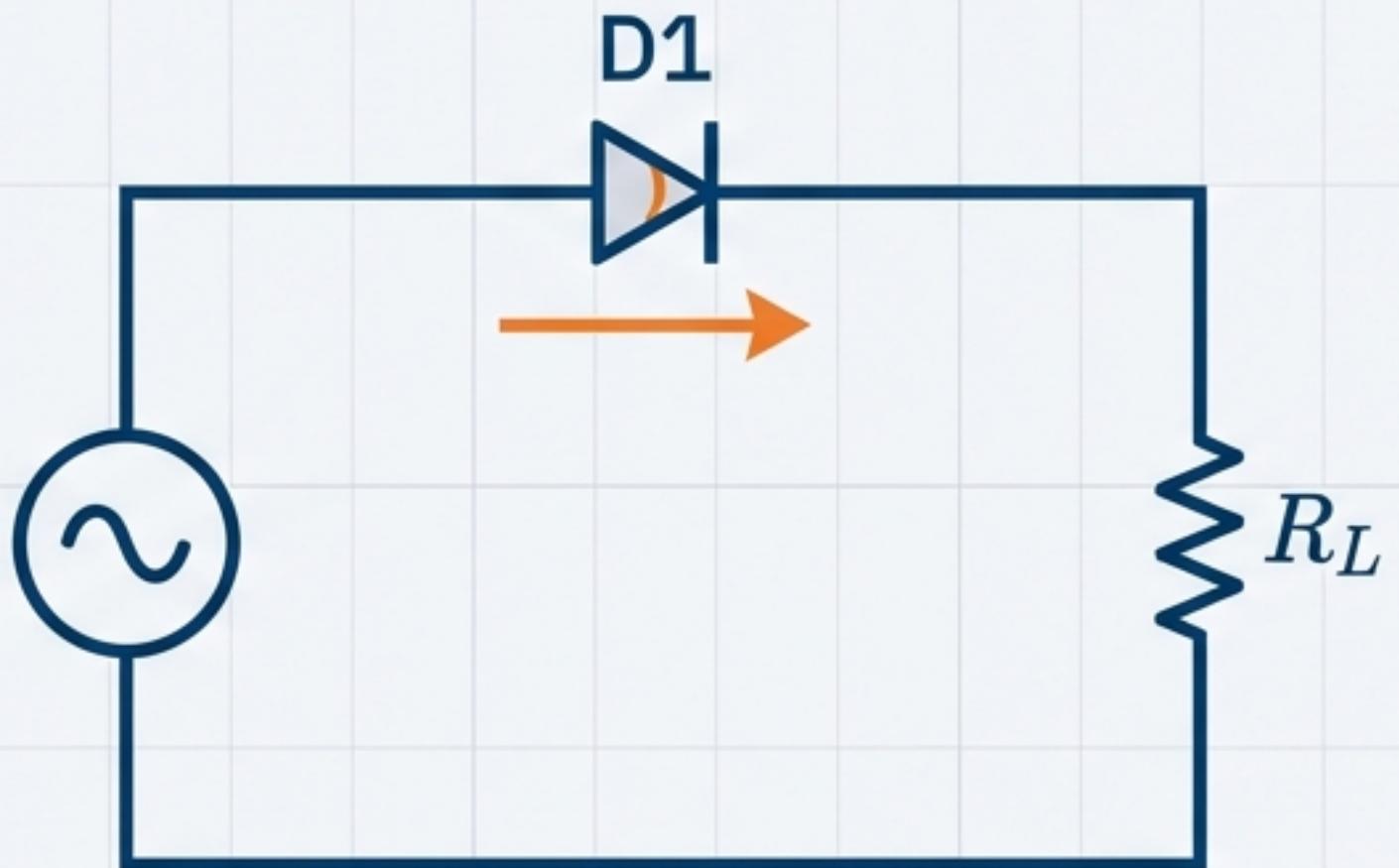

Inefficient: 50% power discarded.

$$V_{dc} = 0.318 \times V_{peak}$$

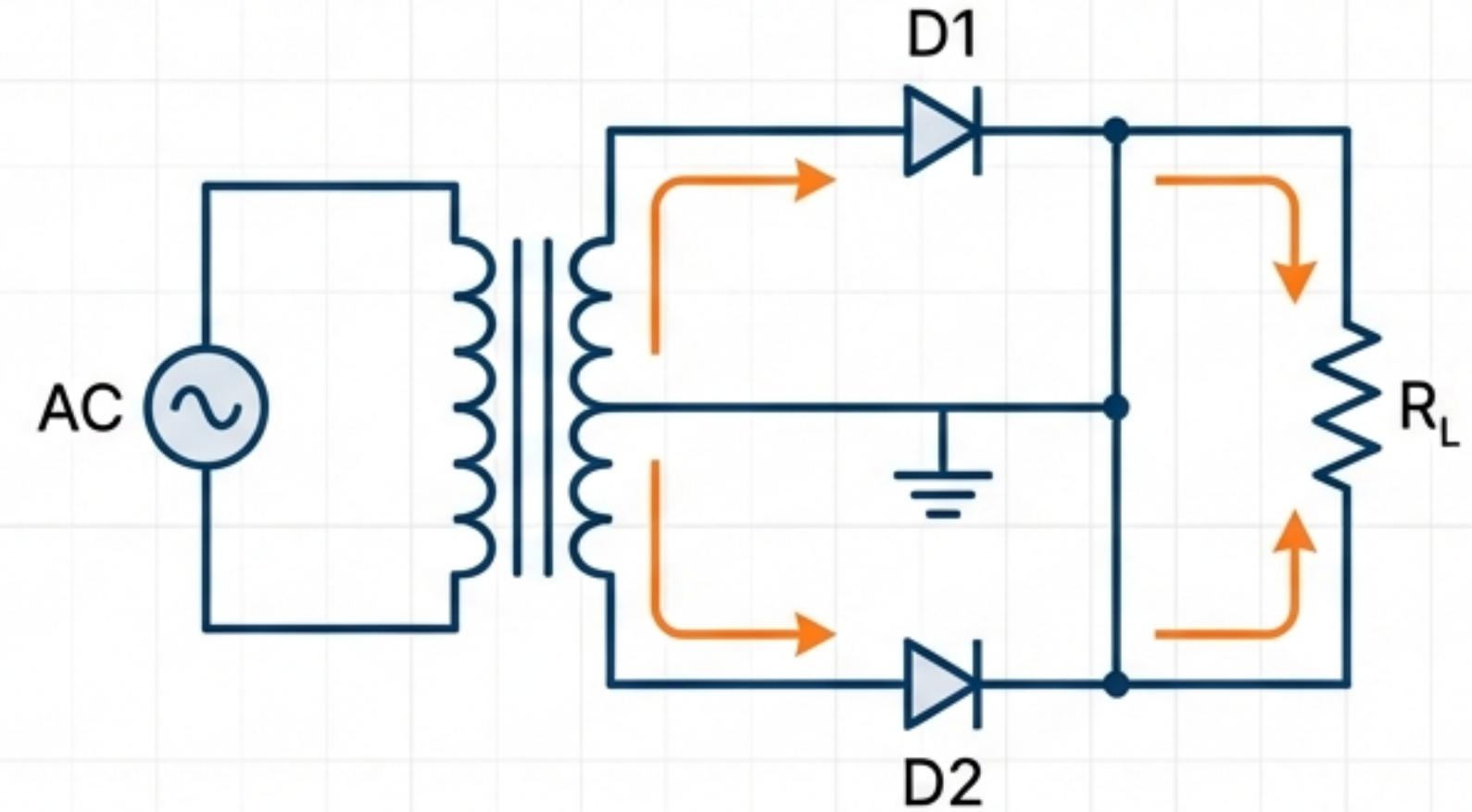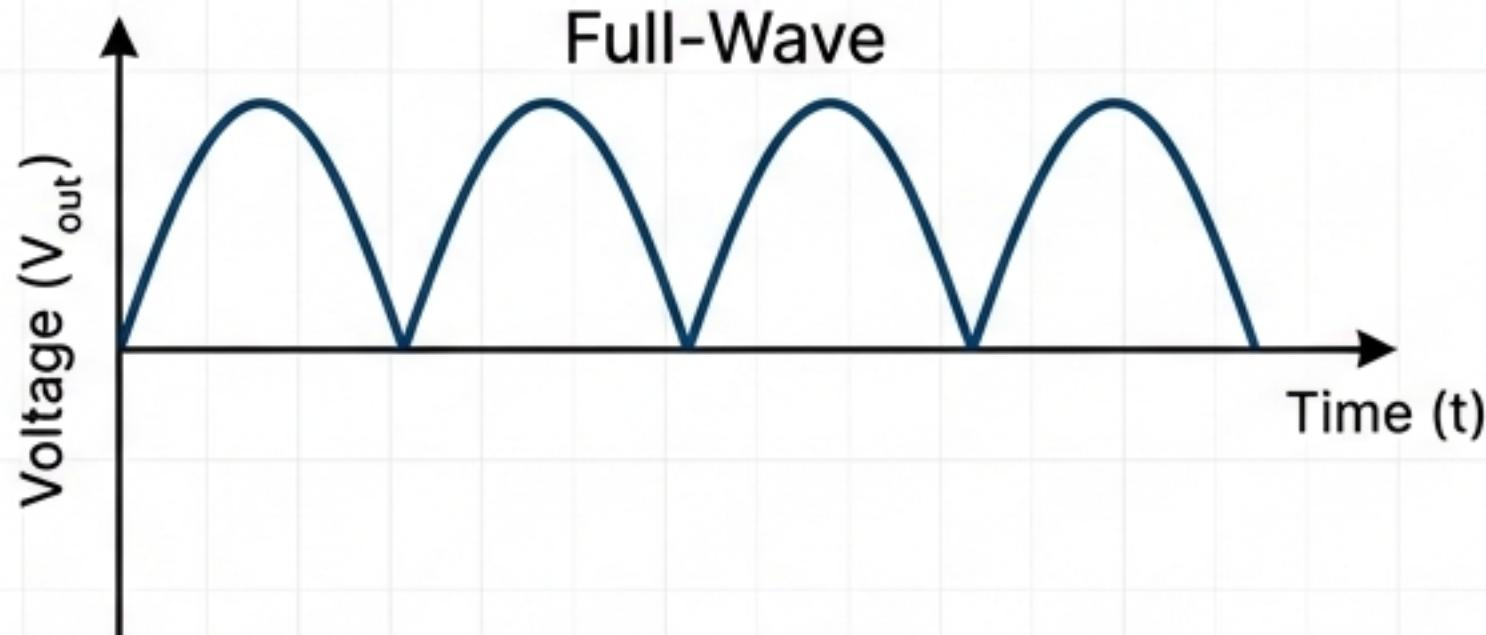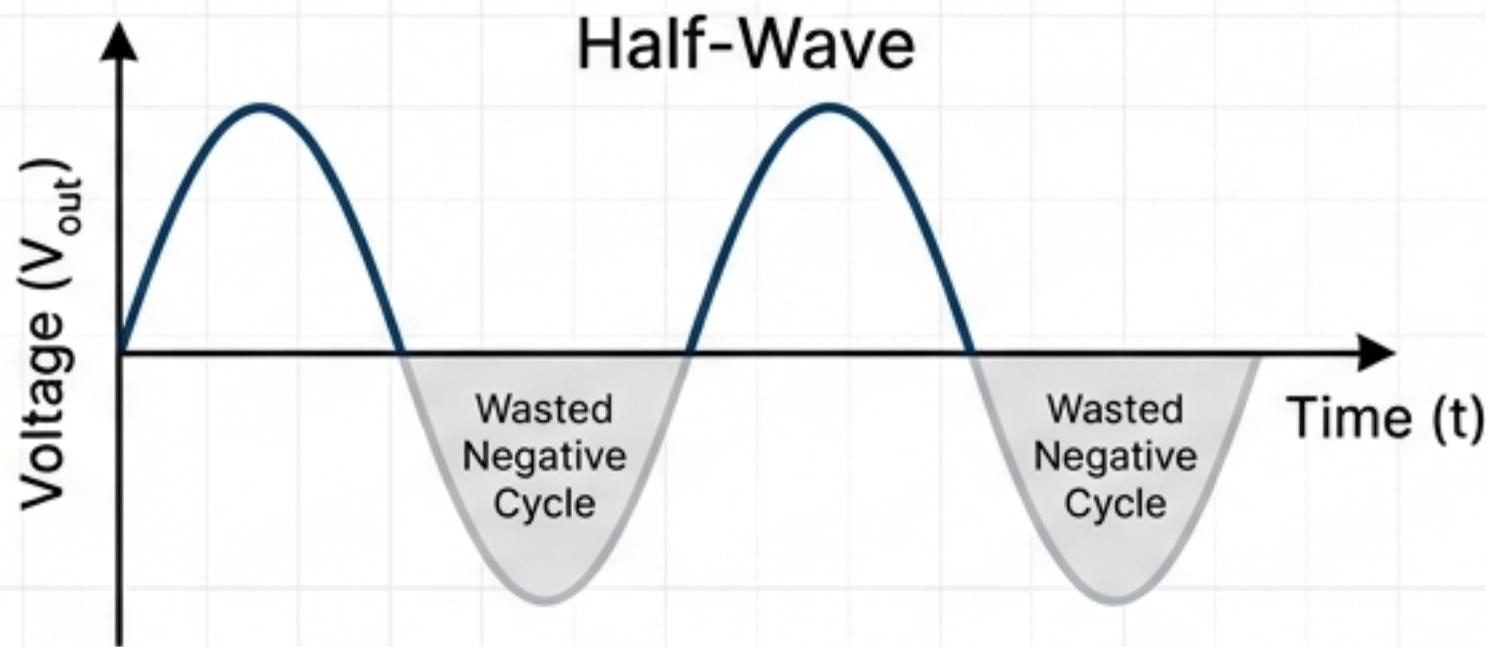
Closing the Gaps: Full-Wave Rectification



- Utilizes both AC half-cycles.
- Method A: Centre-Tapped Transformer (2 Diodes).
- Method B: Bridge Rectifier (4 Diodes - Industry Standard).


Industry Standard: The Bridge Rectifier

Positive Cycle:
Current via D1 & D3.

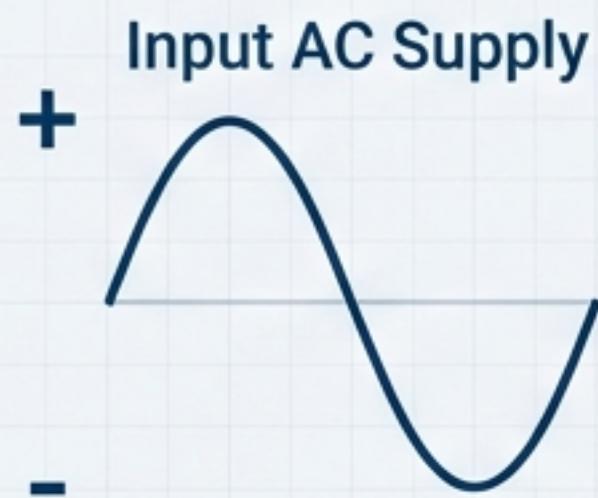


Positive Cycle:
Current via D1 & D3.

Negative Cycle:
Current via D2 & D4.


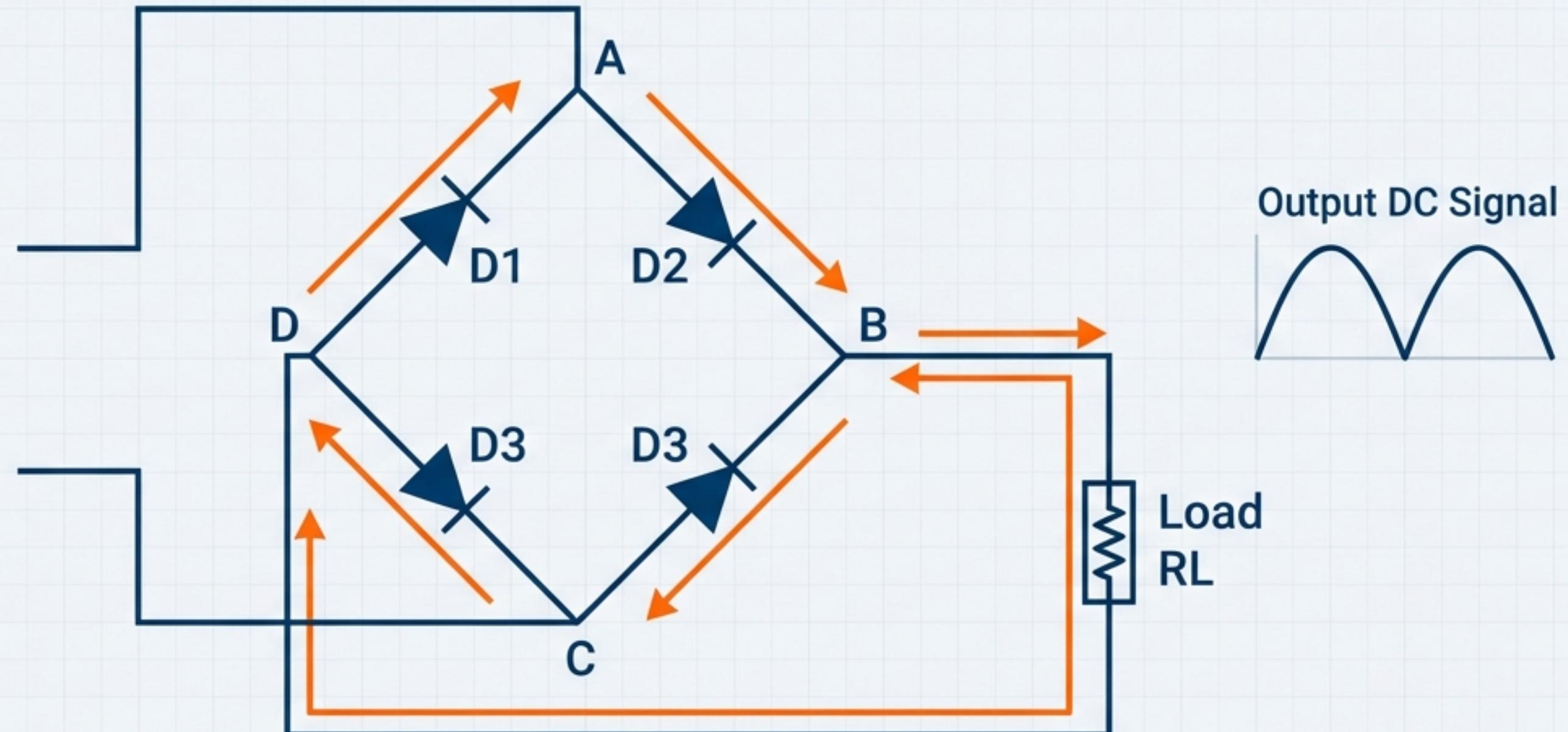


Crucial Outcome: Current always flows through load in the same direction.

The Numbers: Half-Wave vs. Full-Wave

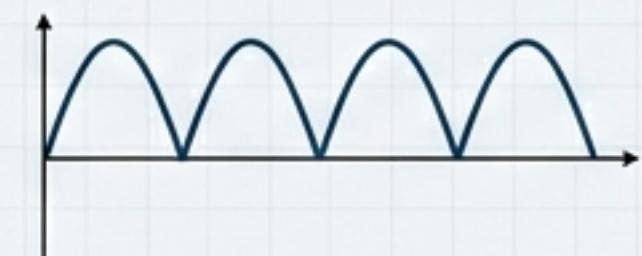	Half-Wave	Full-Wave
Average DC Voltage (Vdc)	$0.318 \times V_{peak}$	$0.637 \times V_{peak}$ (Doubles) 
Ripple Frequency	50Hz (Hard to smooth)	100Hz (Easier to smooth) 
Efficiency	Low (Wasted Cycle) 	High 



Smoothing the Pulses

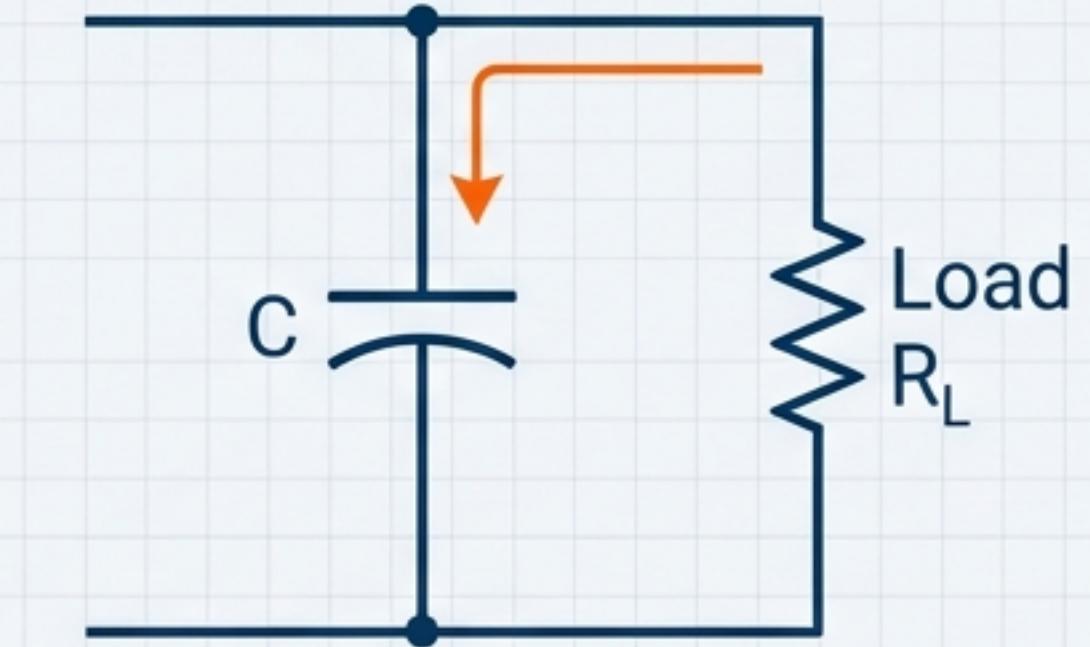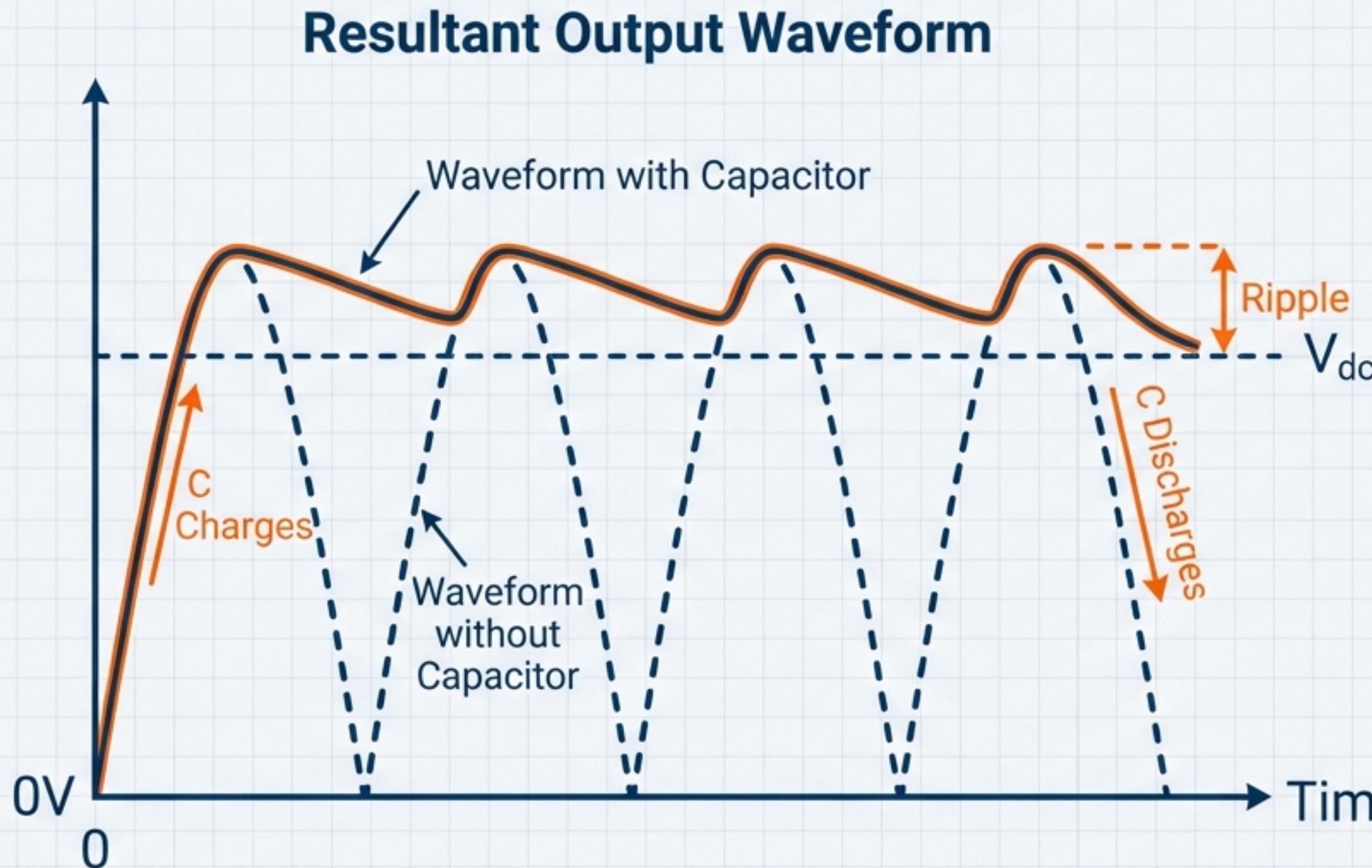

The Reservoir Effect:
Capacitor charges on peak,
discharges during drops.

Goal: Fill the valleys to
create a steady line.

Precision Control: Voltage Regulation

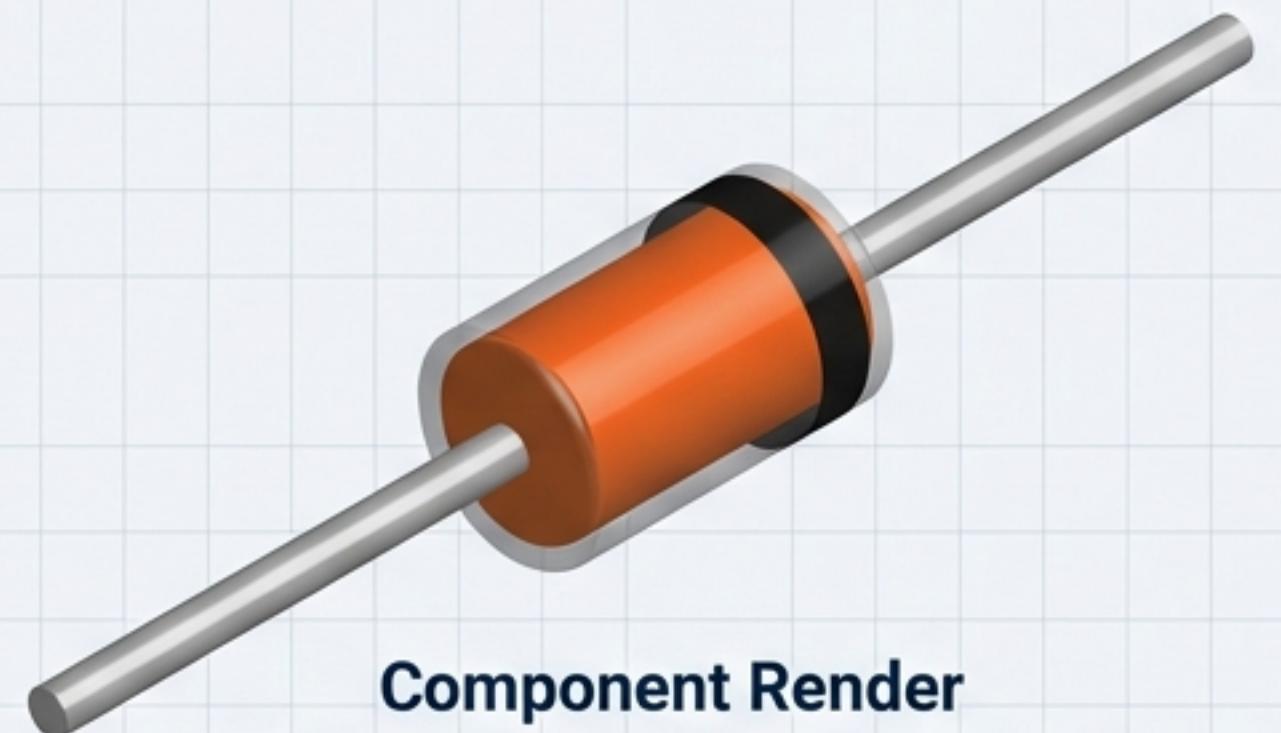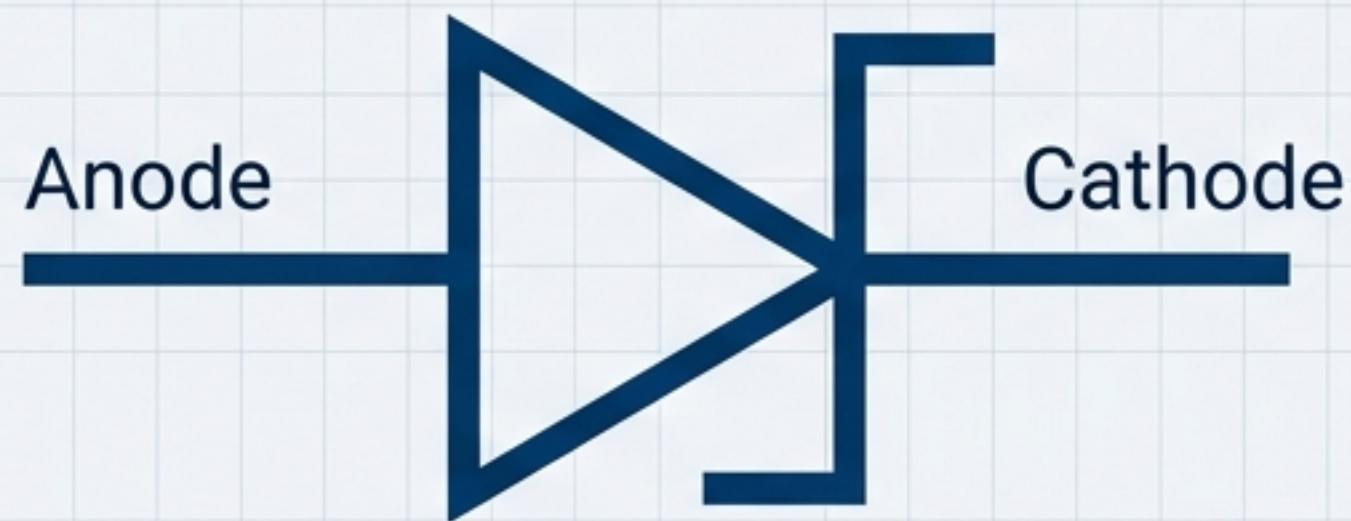

Component Render
Orange Glass with Black Band

- **The Zener Diode:** Operates in **Reverse Breakdown**.
- **Analogy:** A **Pressure Relief Valve**.
- **Function:** **Clamps voltage** at a set level (e.g., 5.1V) regardless of input fluctuation.
- **Configuration:** Connected in **Reverse Bias** (Parallel to load).

Calculating Zener Protection



The Zener needs a **Series Resistor** (R_S) to limit current and prevent destruction.

$$R_S = \frac{V_{supply} - V_{zener}}{I_{total}}$$


V_{supply} : Unregulated Input

V_{zener} : Regulated Output

I_{total} : Total Circuit Current

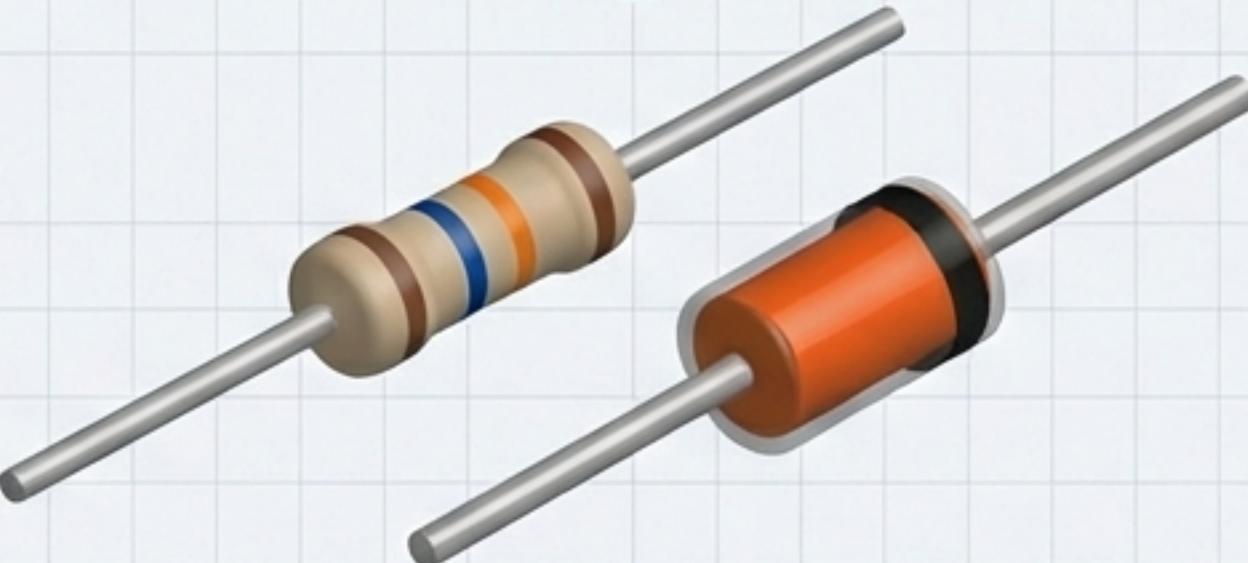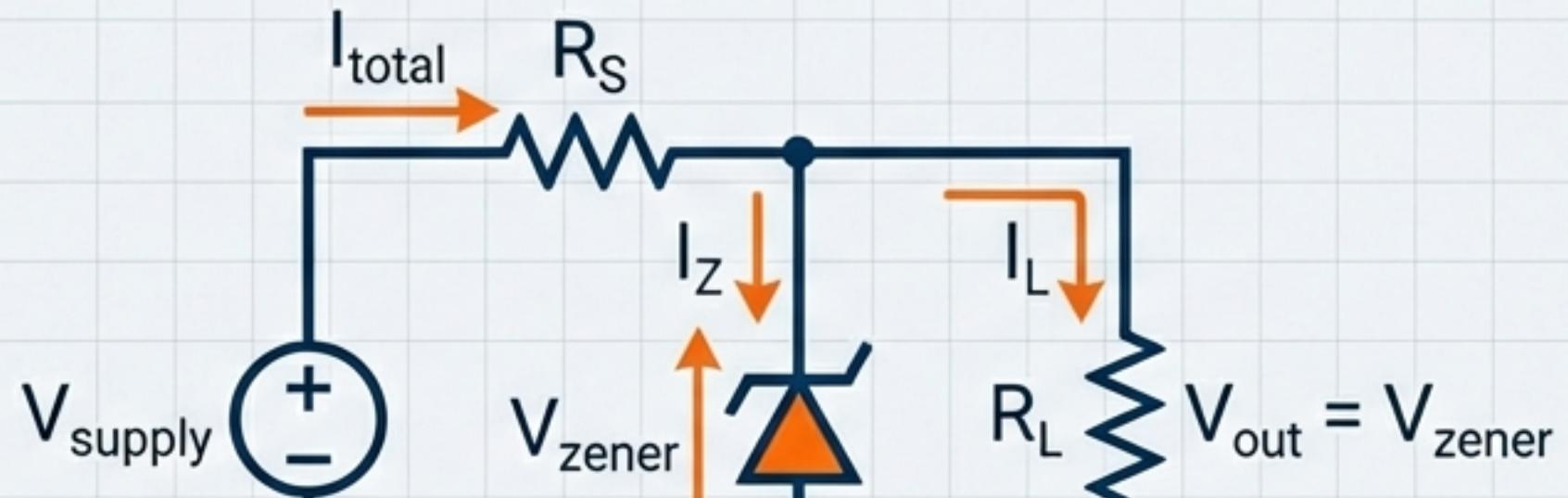

The Complete Power Supply Chain

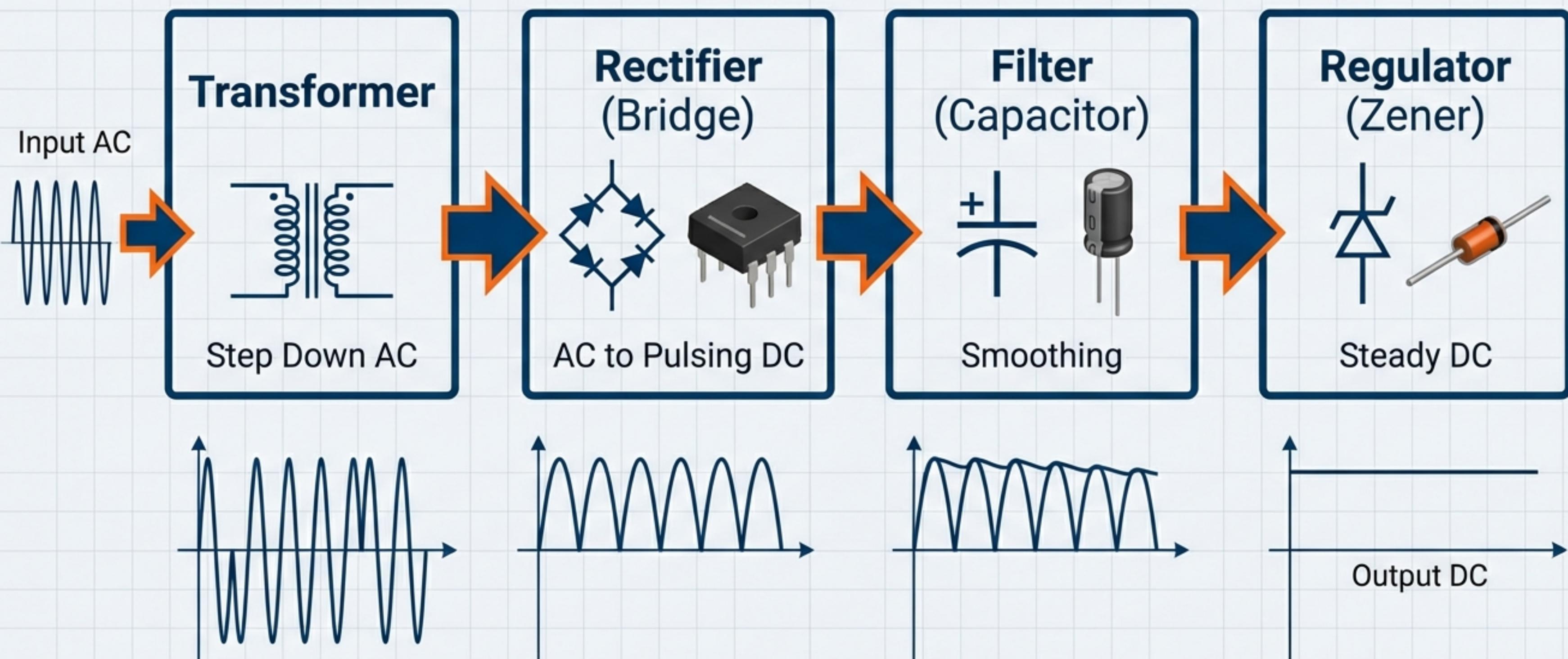


Fault Finding & Diagnostics

Tools



Digital Multimeter

Measures RMS
voltage &
Resistance.

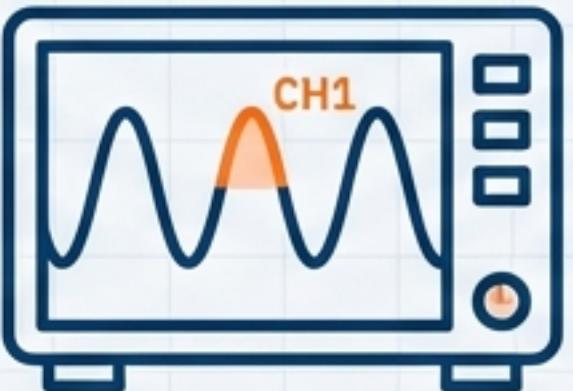

Oscilloscope


Visualizes shape
(Ripple, Distortion)
& Peak Voltage.

Common Faults



Blown Fuse

Suspect Shorted
Diode.

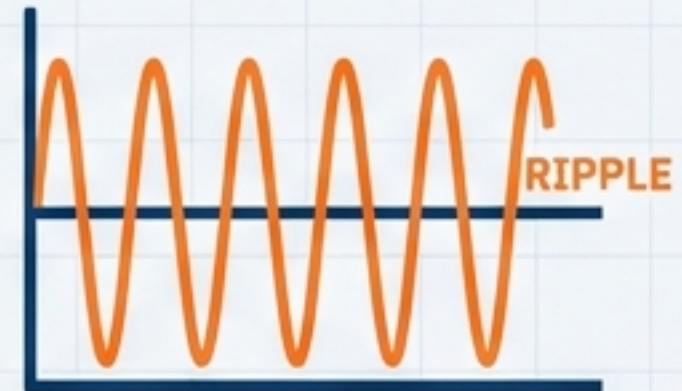


Low/Ripply Output

Suspect Open
Capacitor or Open
Diode.

Exam Note: $V_{peak} = V_{rms} \times 1.414$

Essential Formulas Cheat Sheet

RMS & Peak Voltage

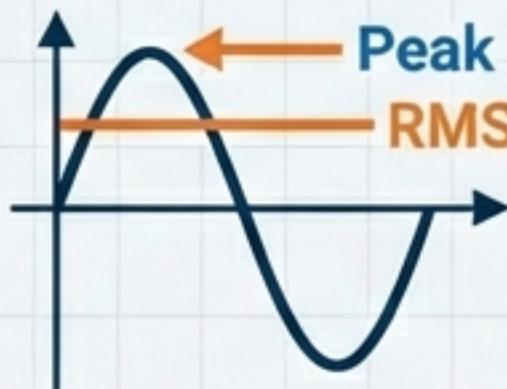


$$V_{rms} = 0.707 \times V_{peak}$$

$$V_{peak} = 1.414 \times V_{rms}$$

DC Output Voltage

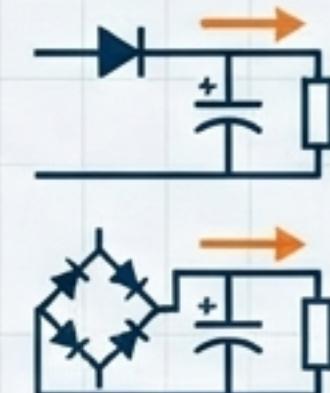
Half-Wave: $V_{dc} = 0.318 \times V_{peak}$



Full-Wave: $V_{dc} = 0.637 \times V_{peak}$

Fundamental Laws


Ohm's Law: $I = V/R$

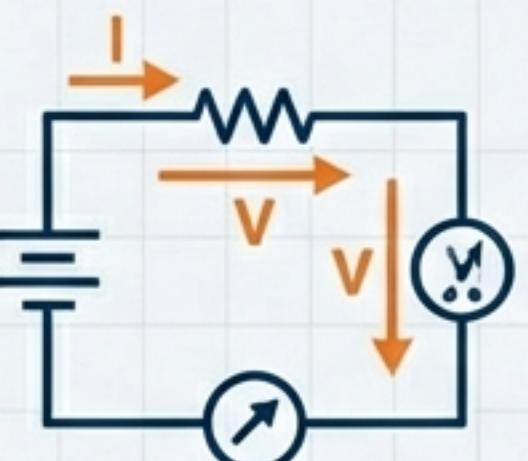


Power: $P = V \times I$

Frequency & Period

$$f = 1/T$$

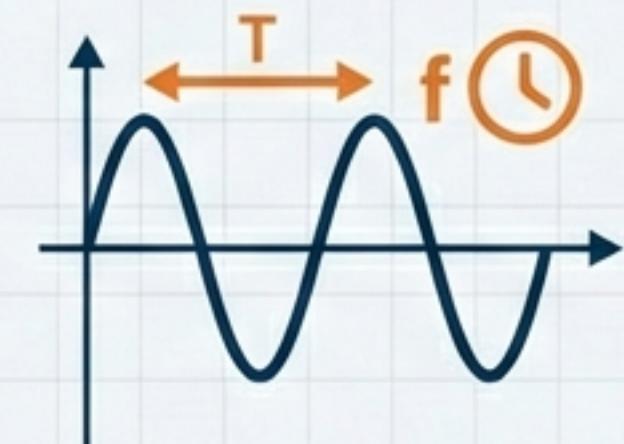

Power Transformed

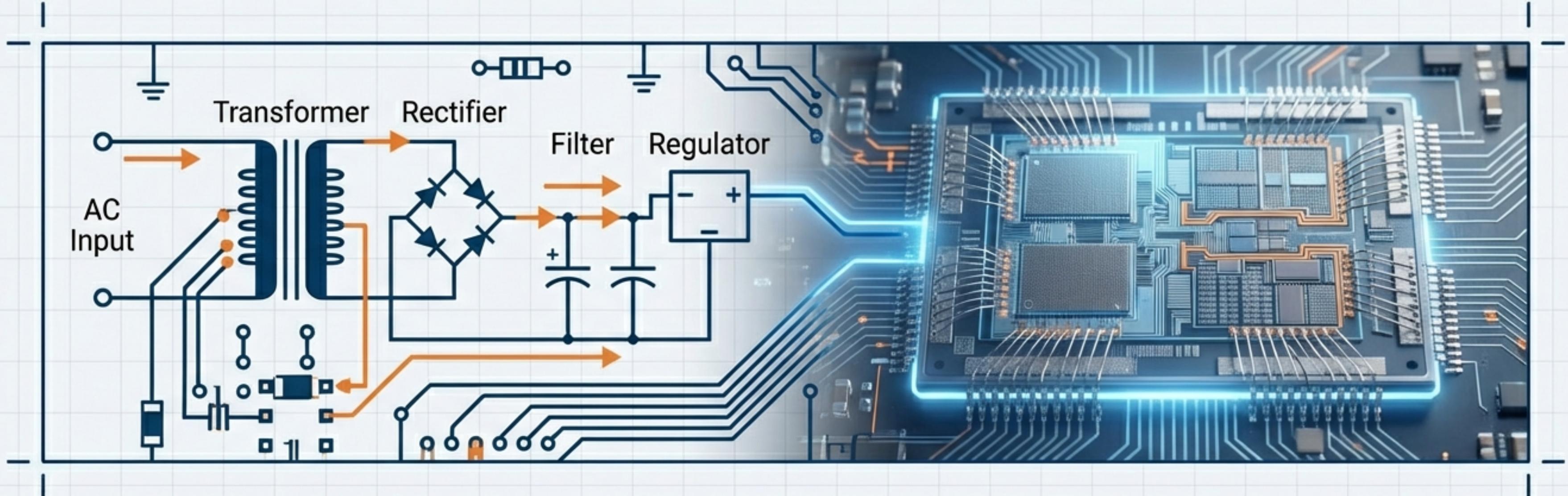

From dangerous AC to precision DC.

Process: Transformer → Rectifier → Filter → Regulator

Ready for Questions.