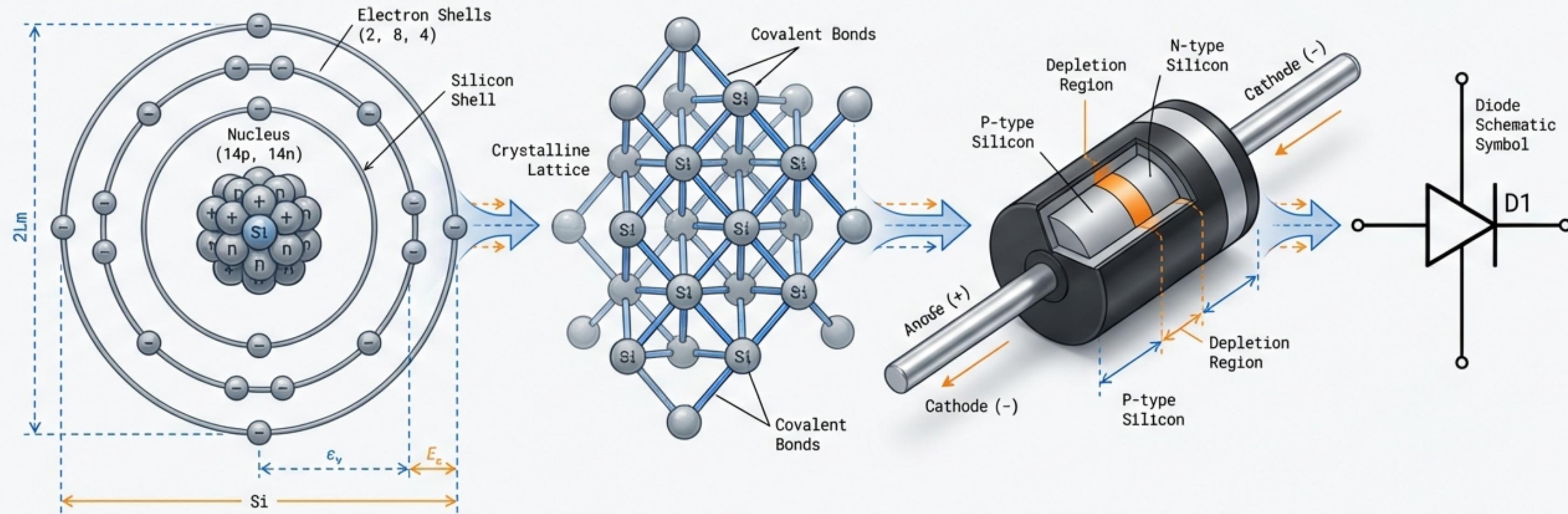



# Unit 11: Semiconductors and Diodes

From Atomic Theory to Circuit Application



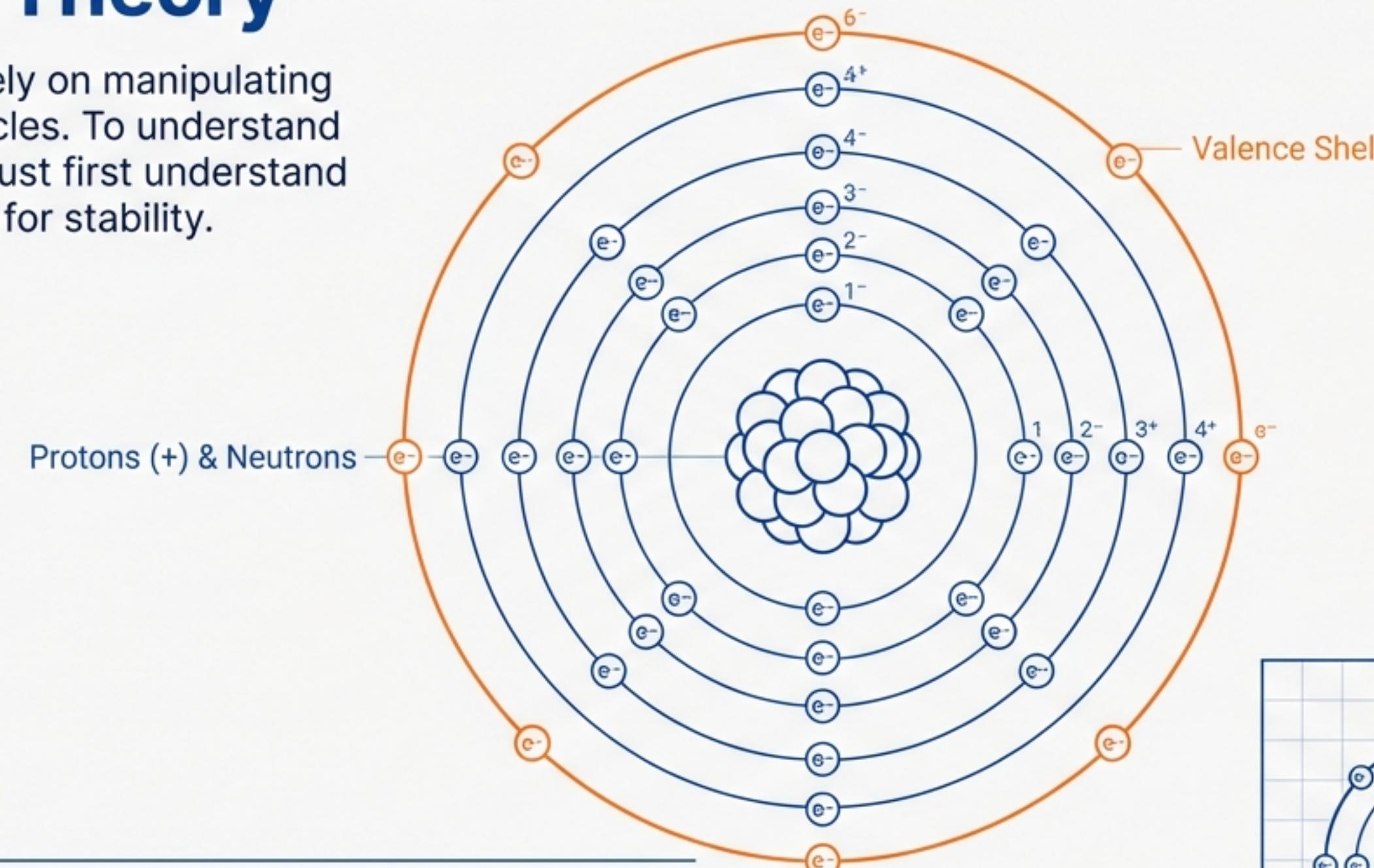
# The Physics of Matter: Atomic Theory


All electronics rely on manipulating subatomic particles. To understand the diode, we must first understand the atom's drive for stability.



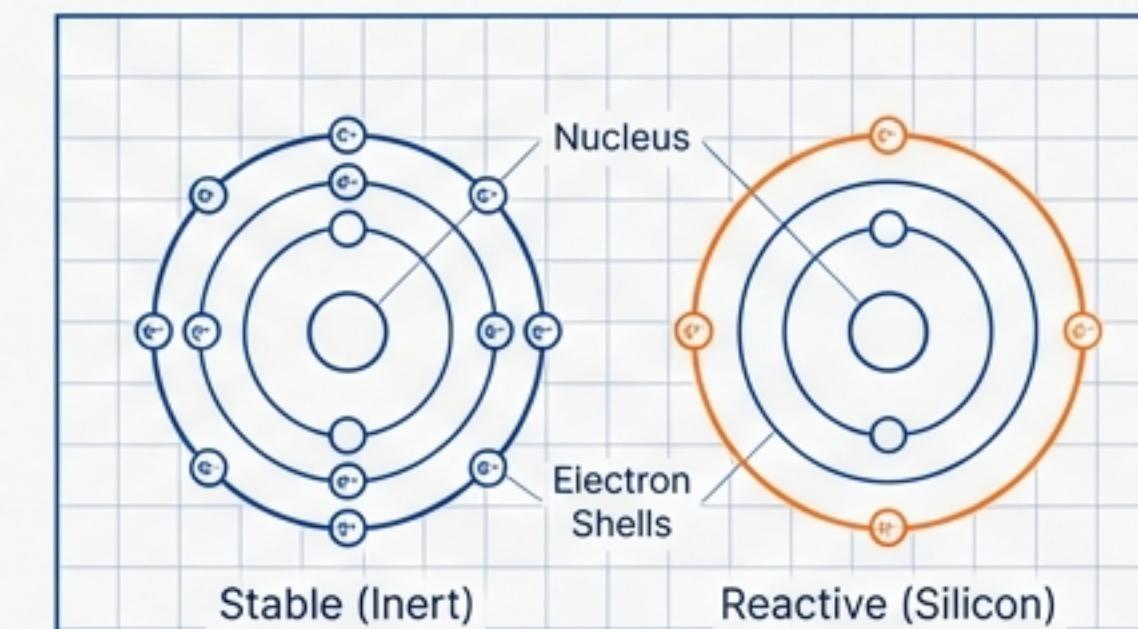**The Octet Rule:** Atoms seek stability by attempting to fill their valence shell with exactly 8 electrons. This drive creates chemical bonding and electrical flow.



# The Spectrum of Conductivity

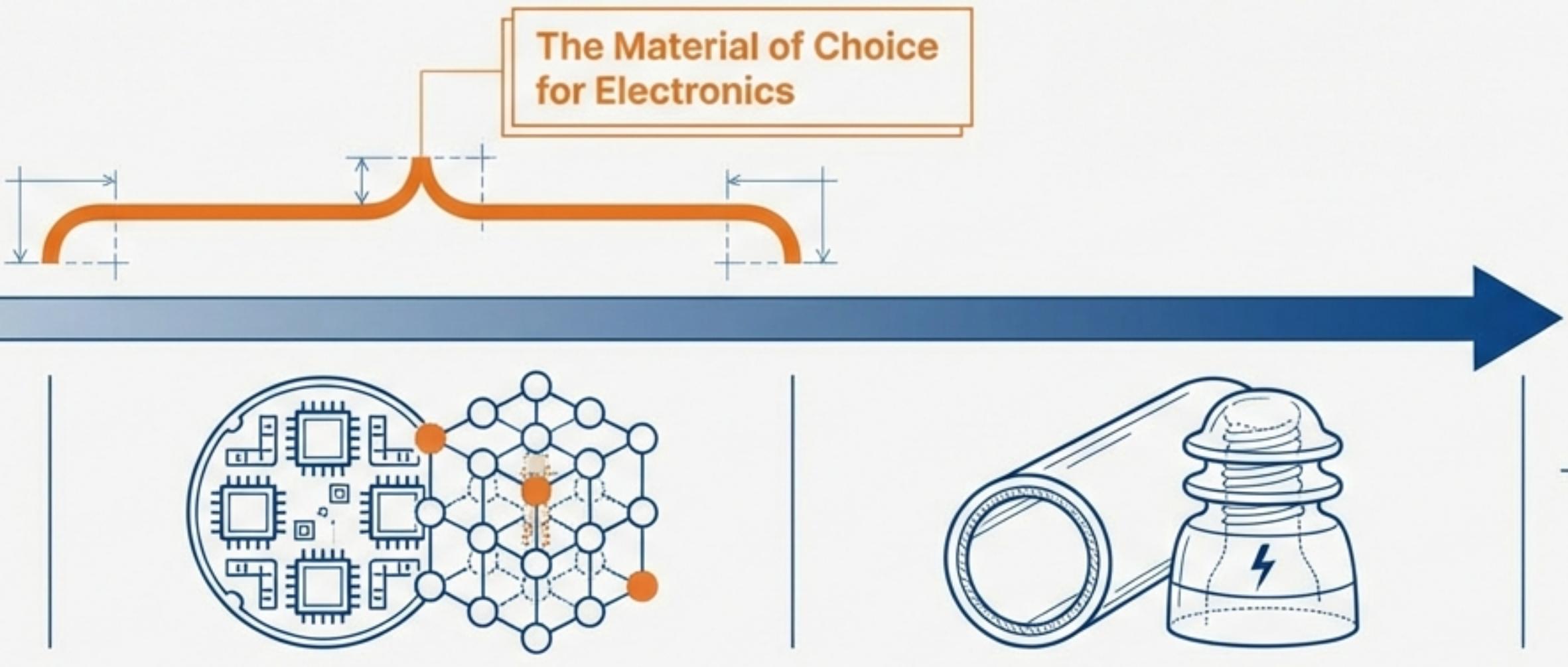

## Conductors

1–3 Valence Electrons.

Loosely held.

Examples: Copper, Gold, Aluminium

## Semiconductors

Exactly 4 Valence Electrons.

Conductivity controlled by doping.

Examples: Silicon, Germanium

## Insulators

5–8 Valence Electrons.

Tightly held.

Examples: PVC, Glass, Rubber

Low (Left)


Electrical Resistance

High (Right)

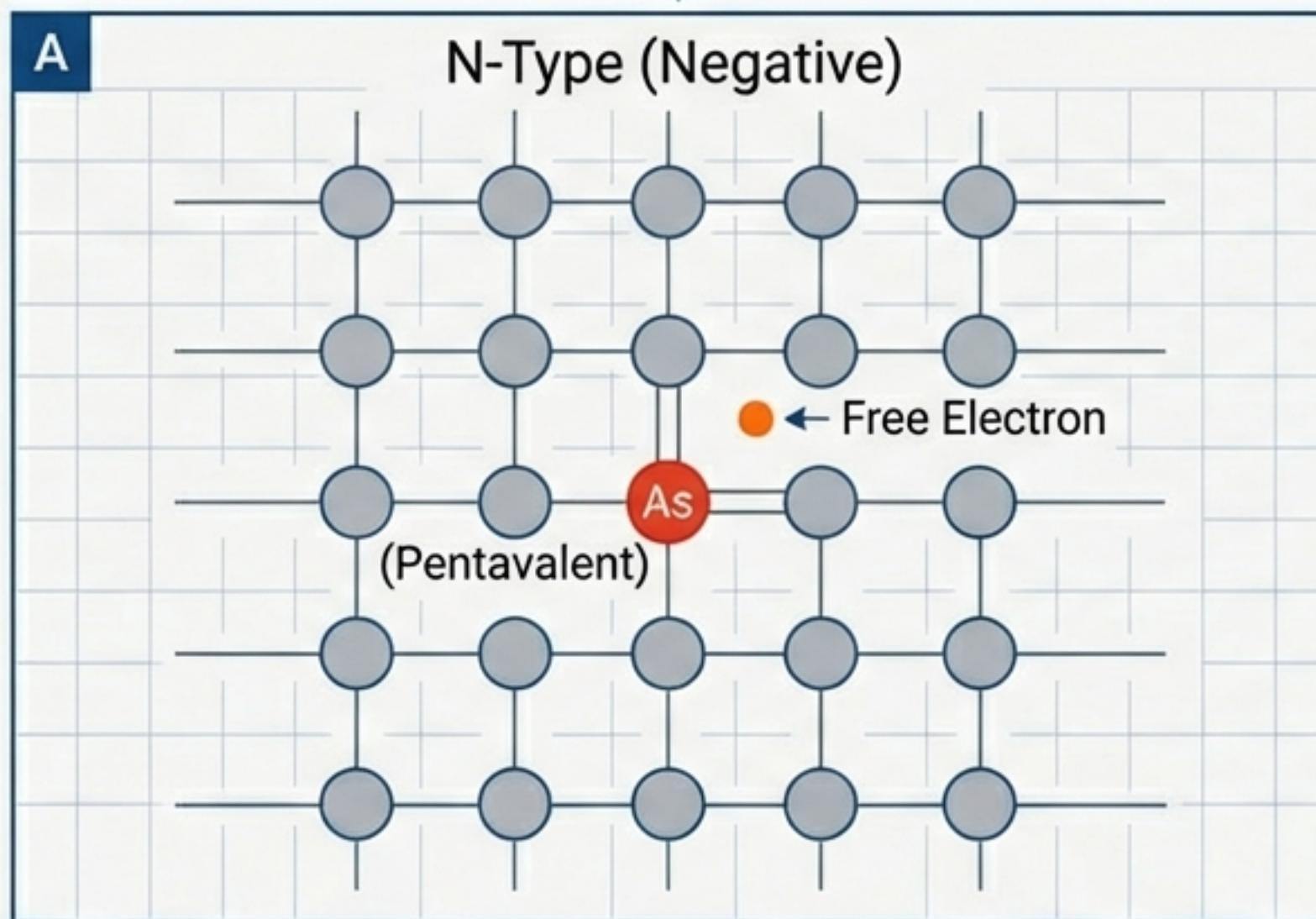
# Engineering Conductivity: The Doping Process

Transforming intrinsic silicon into N-Type and P-Type materials.

Pure silicon acts as an insulator. By adding impurities ("Doping"), we introduce instability that creates charge carriers.




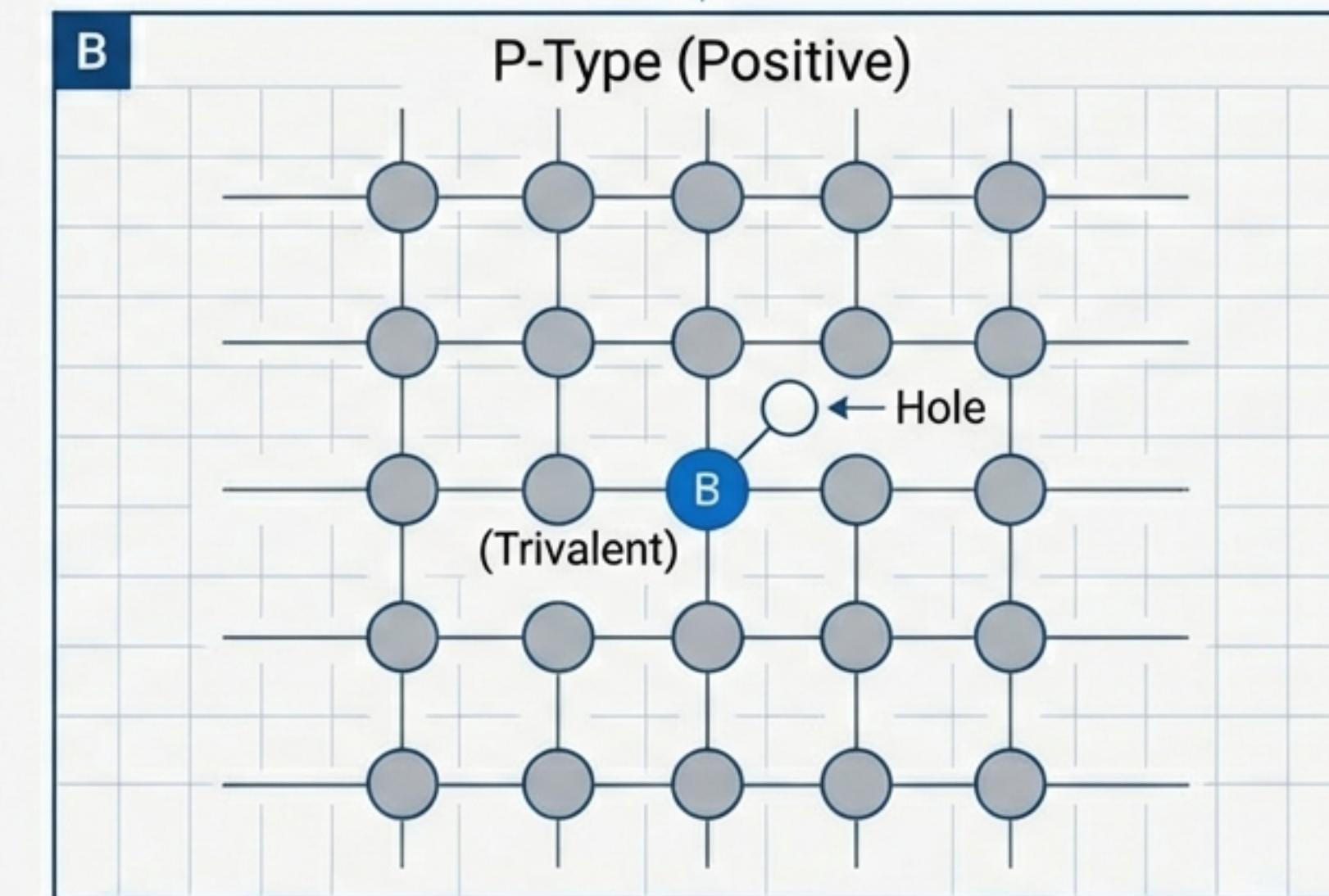Pentavalent Impurity ( $5e^-$ ). Result: Excess Electrons.



Trivalent Impurity ( $3e^-$ ). Result: Excess Holes.


# The PN Junction: Creating the Barrier

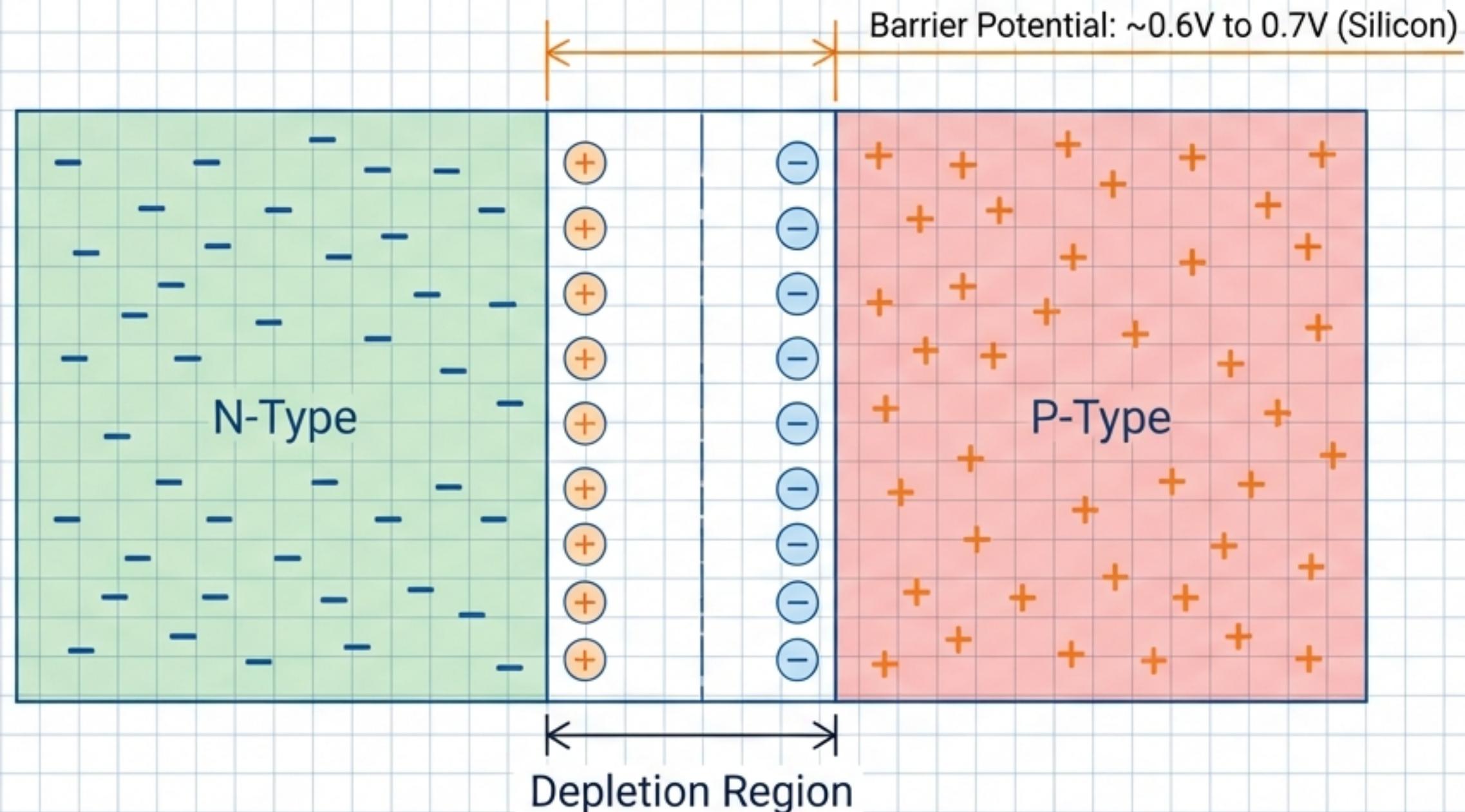

## Process Description:


1. **Diffusion:** Electrons rush to fill holes. →→
2. **Recombination:** Charges cancel out. +>-
3. **Isolation:** A wall of ions forms, blocking further flow. →←

# Biassing the Diode (The Switch)

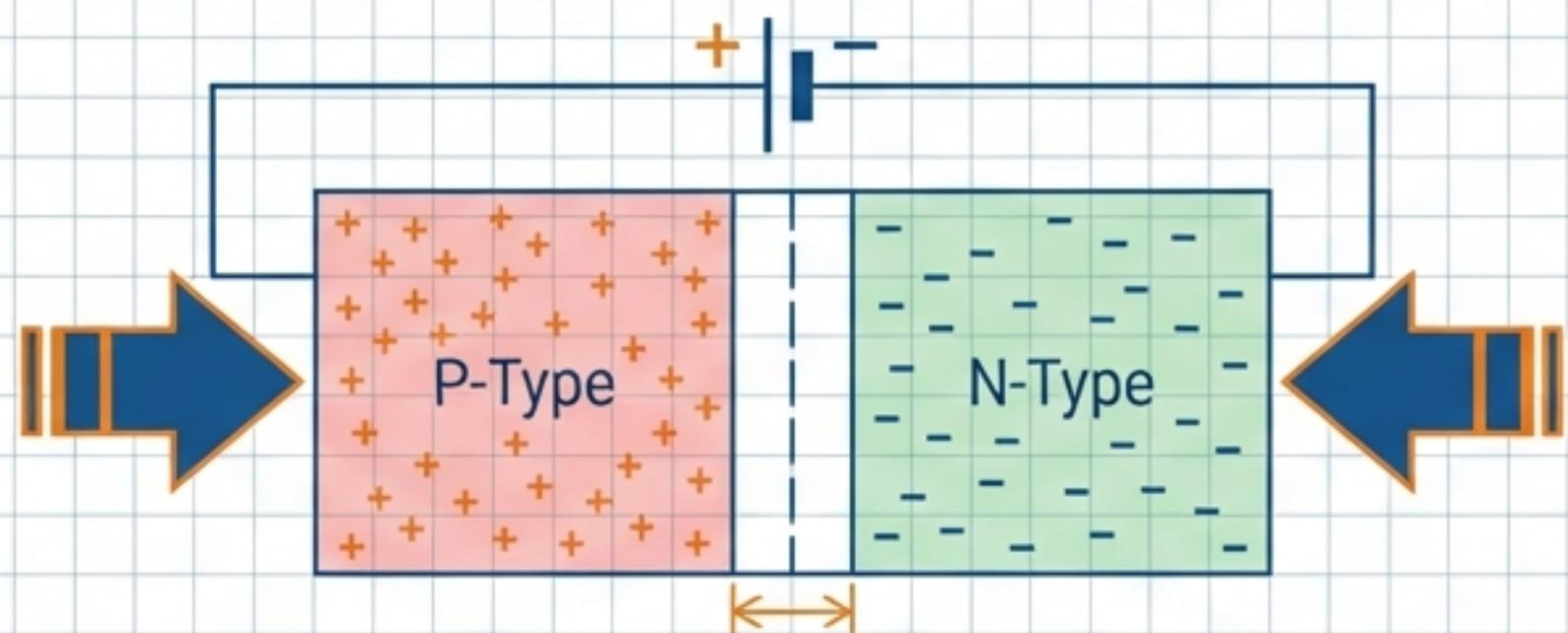
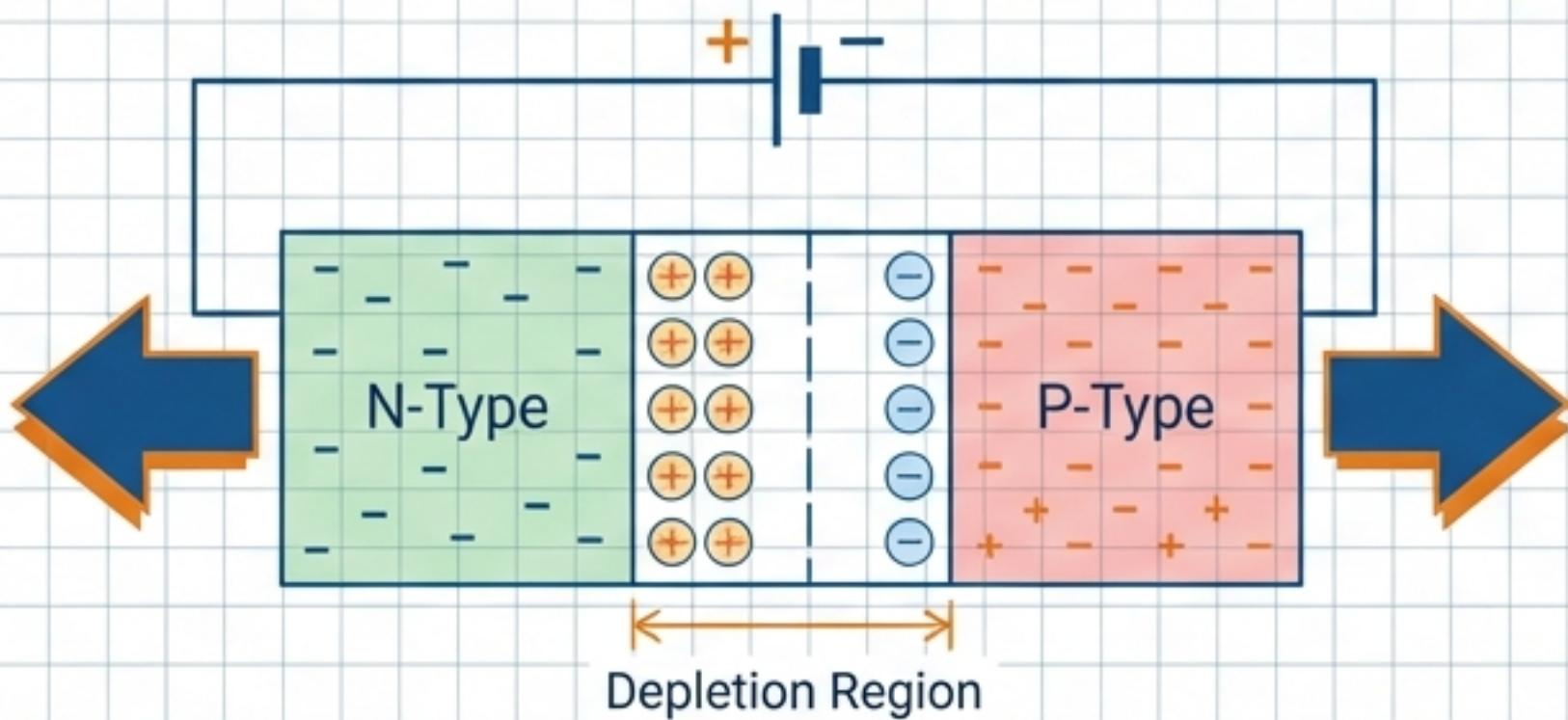
## Forward Bias (Closed Switch)



Current Flows. In Roboto Mono.  
Depletion region narrows.



## Reverse Bias (Open Switch)

Current Blocked. Roboto Mono.  
Depletion region widens.

# Diode Characteristics and Symbols

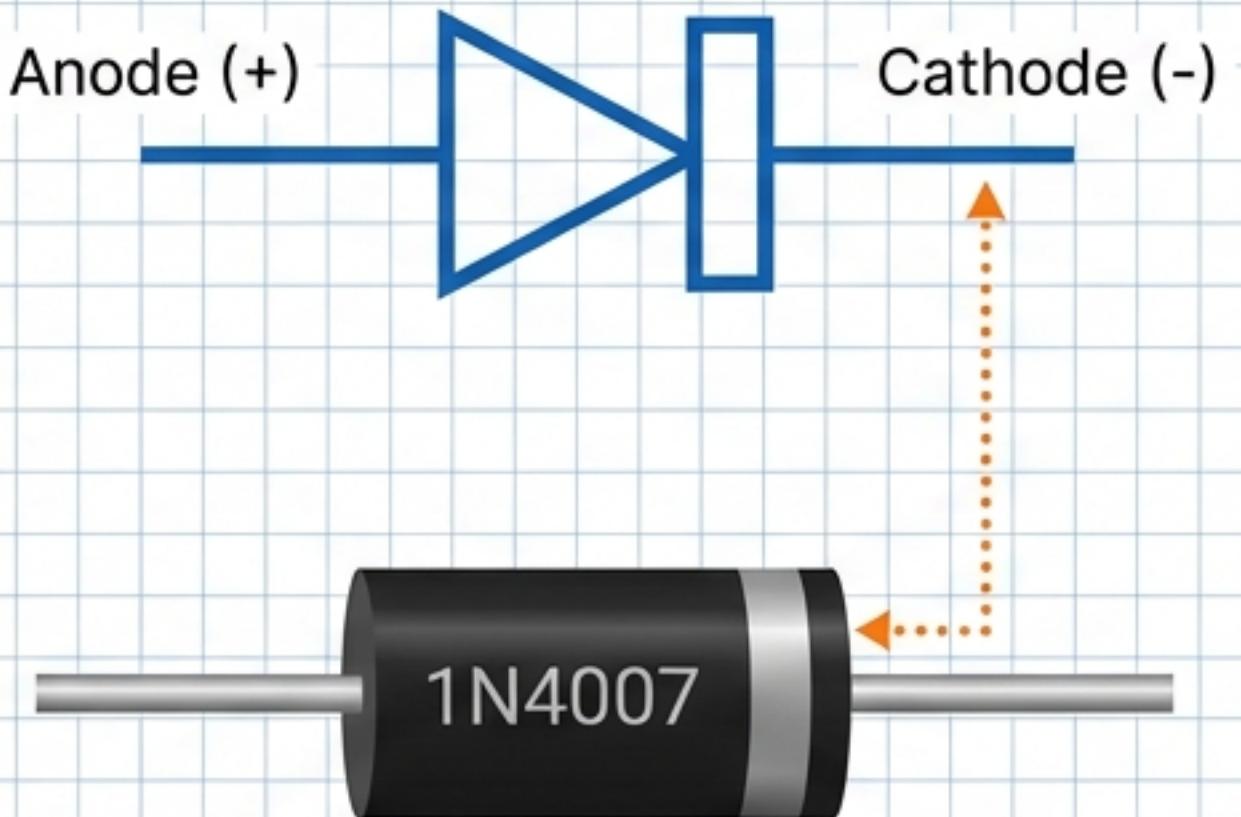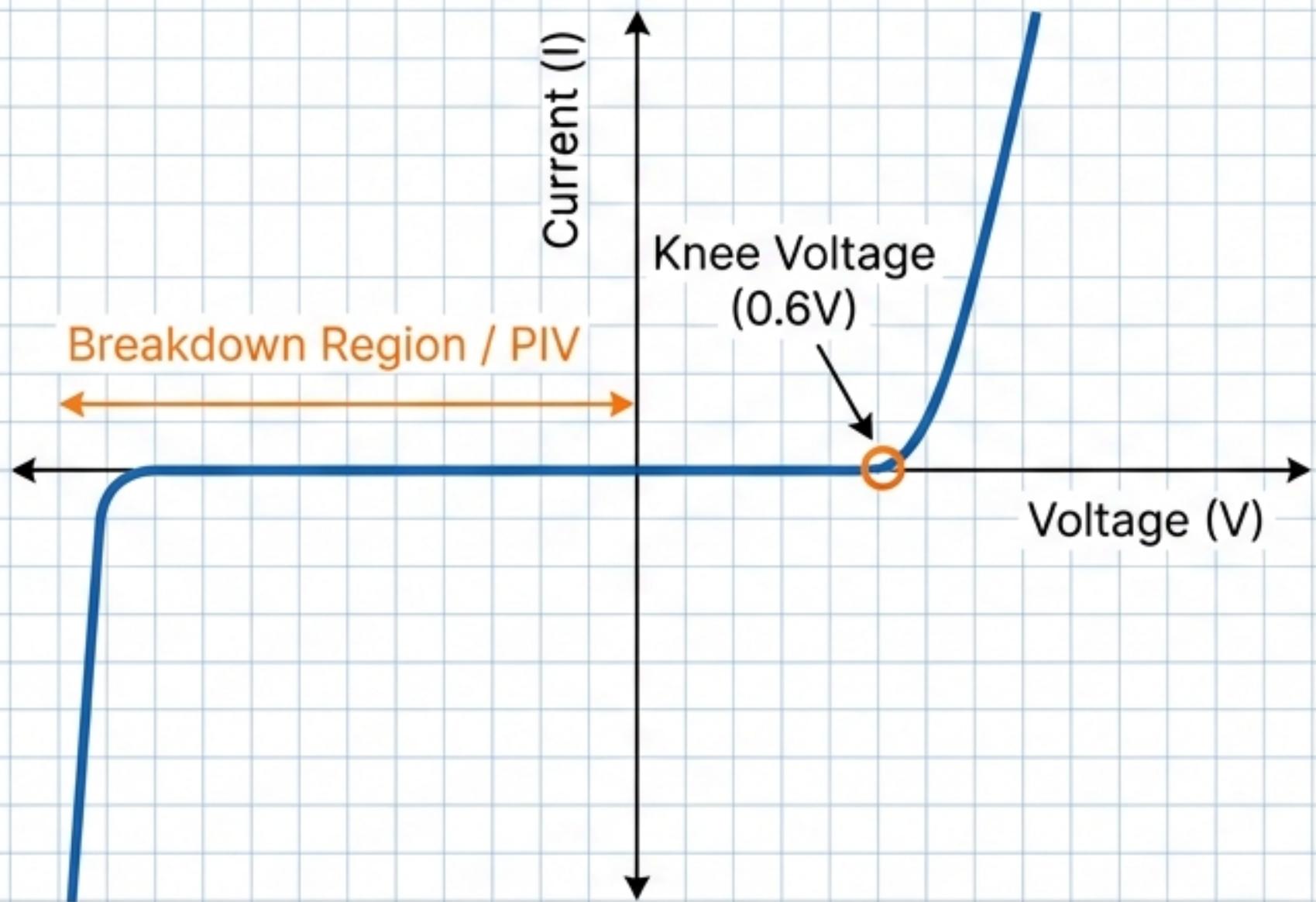


PIV (Peak Inverse Voltage): Max reverse voltage before failure.

If (Max Forward Current): Max current limit.

# Testing Diodes with a Multimeter


**Scenario A (Good Forward)**

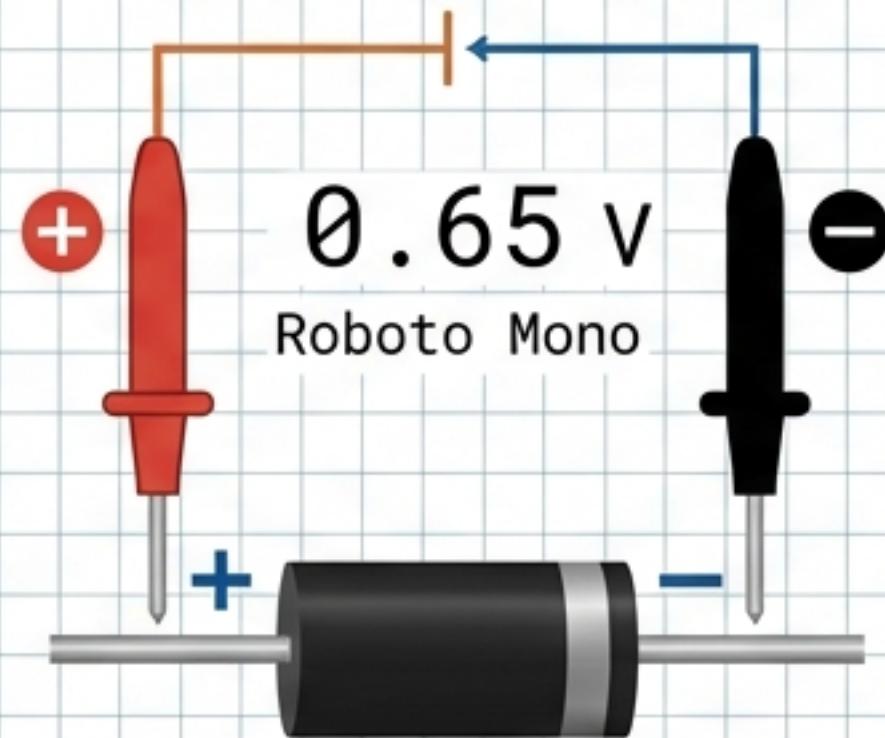

**PASS:** Forward Bias Drop



**Scenario B (Good Reverse)**


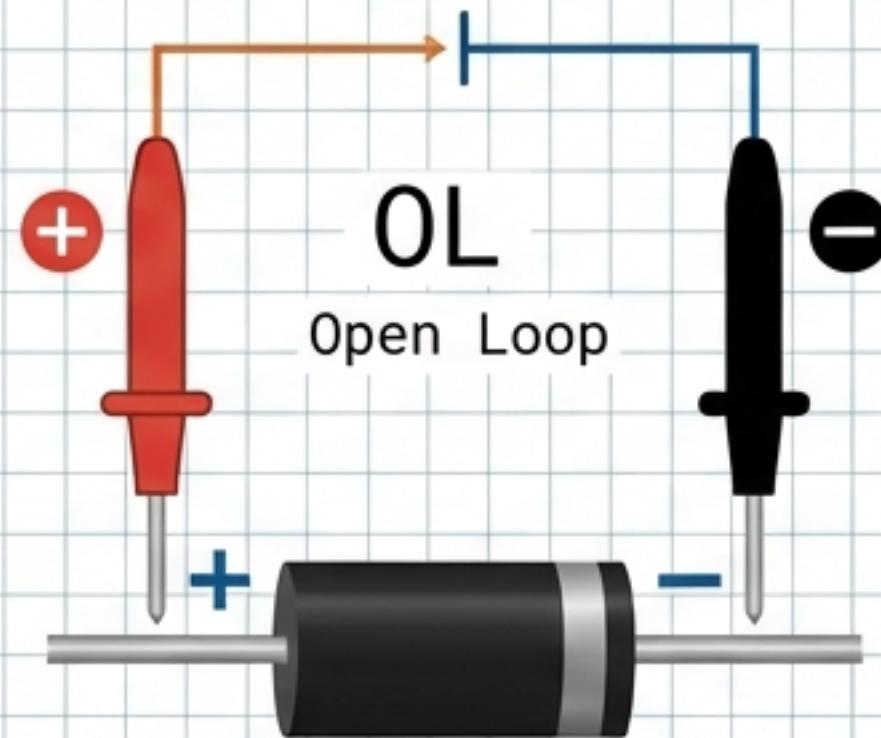


**PASS:** Blocking Current

Short Circuit	Reads 0V / Beep in both directions	FAIL
Open Circuit	Reads OL in both directions	FAIL

# Half-Wave Rectification



Converting AC to DC (Low Efficiency)

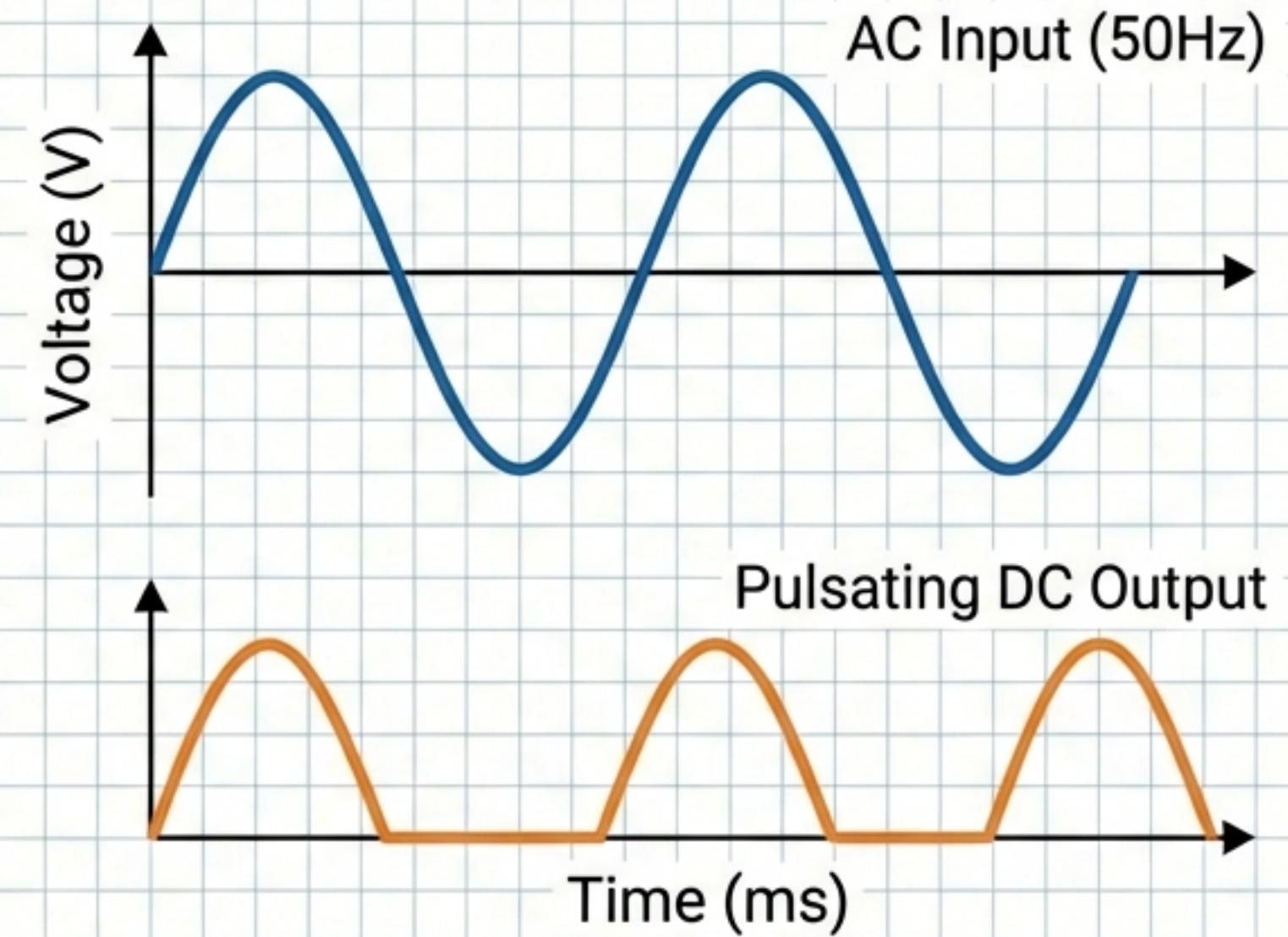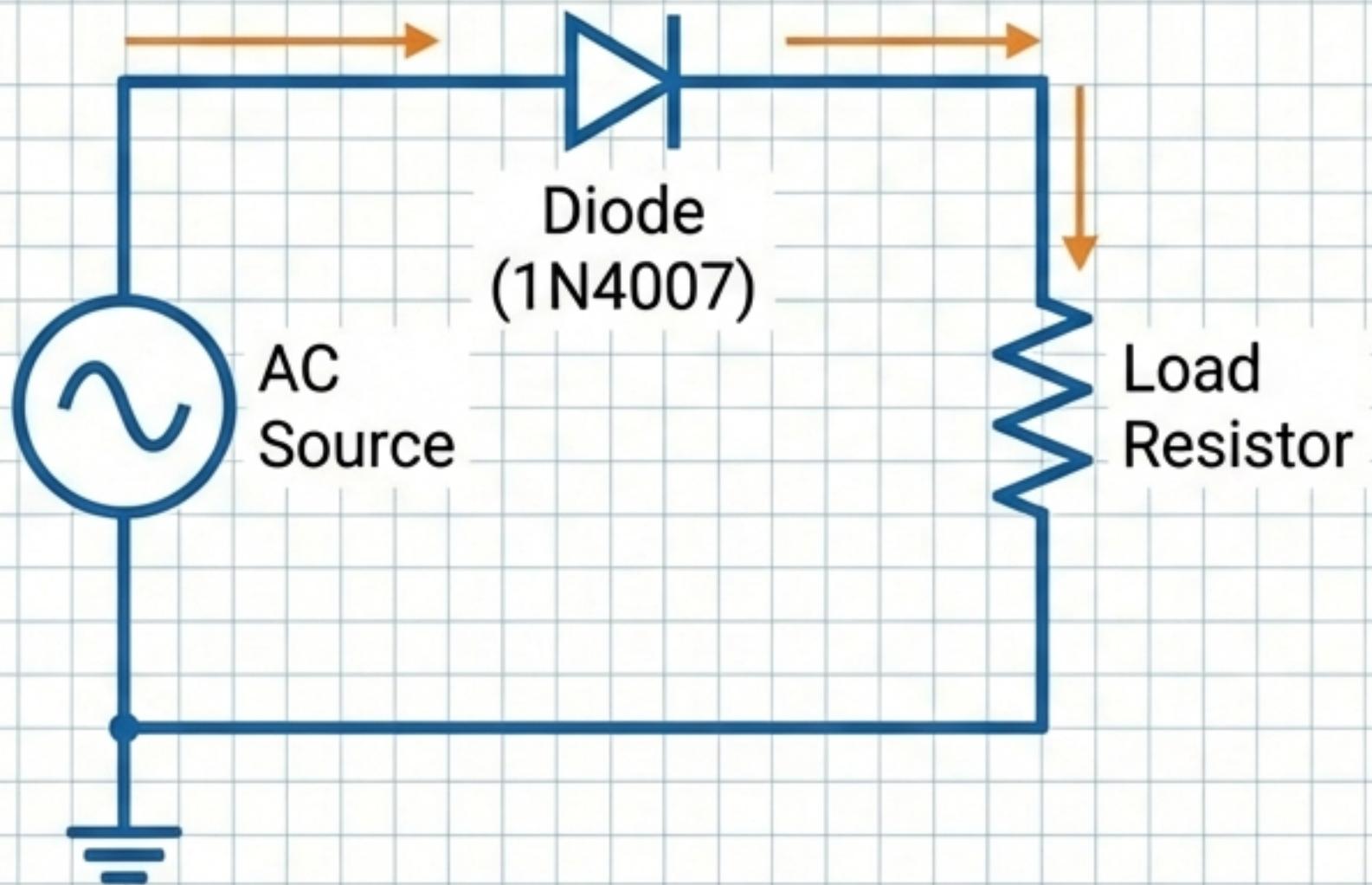

Efficiency: ~50% (Negative cycle is lost)  
Ripple Frequency: 50Hz (Same as Input)



# Full-Wave Bridge Rectification

Converting AC to DC (High Efficiency)

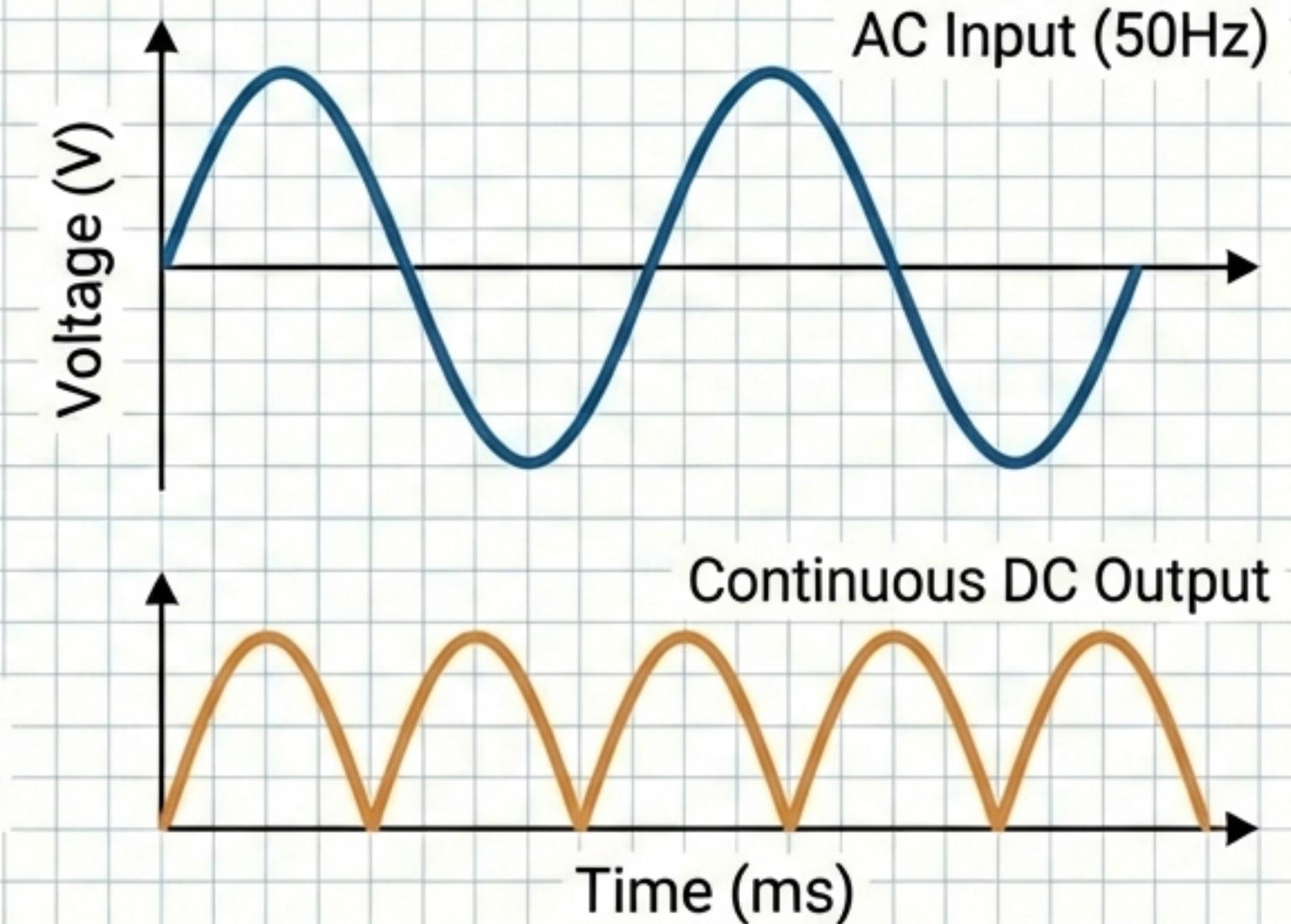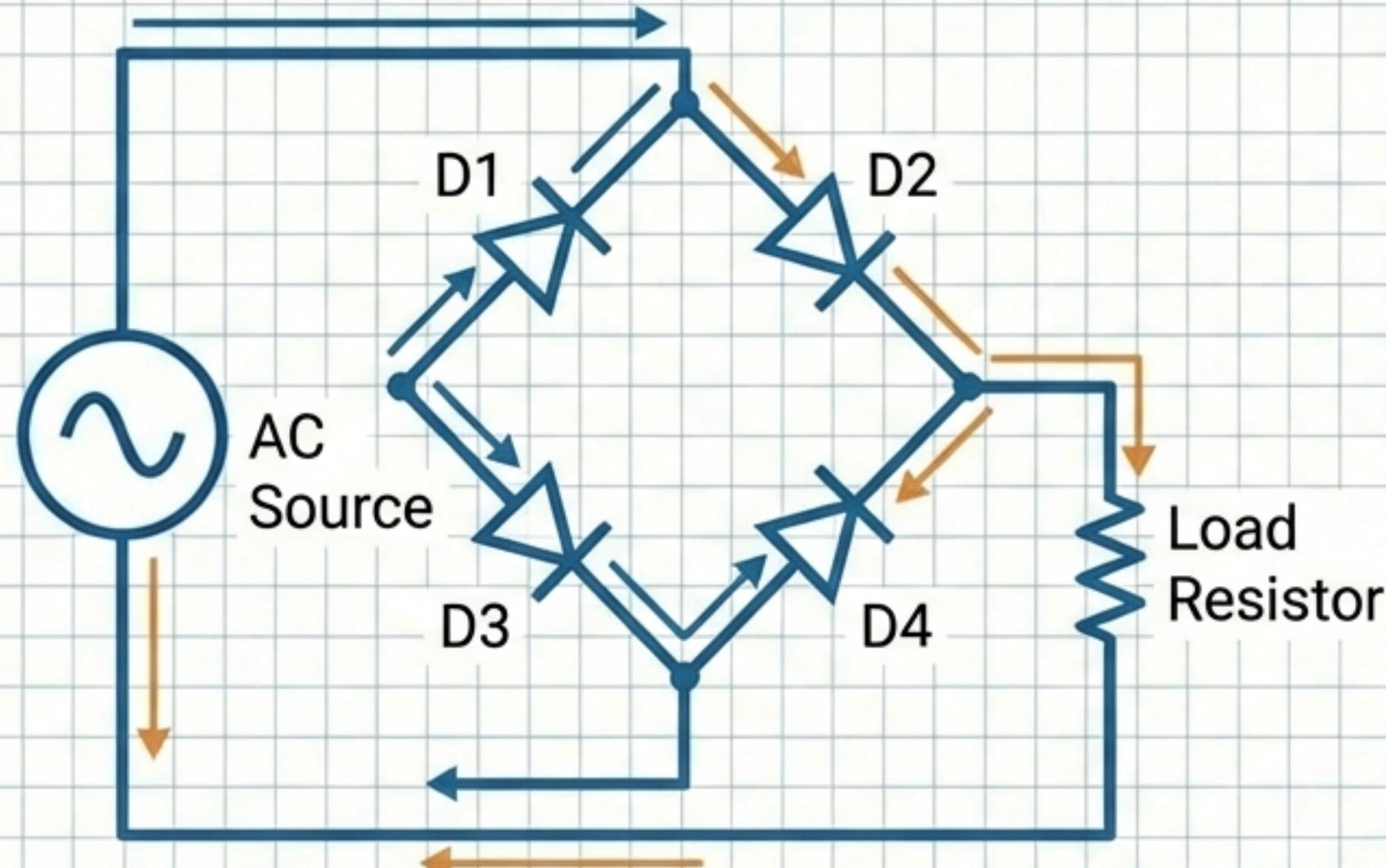

- Efficiency: 100% (Full cycle utilized)
- Ripple Frequency: 100Hz (Double the Input)

# Smoothing the Output

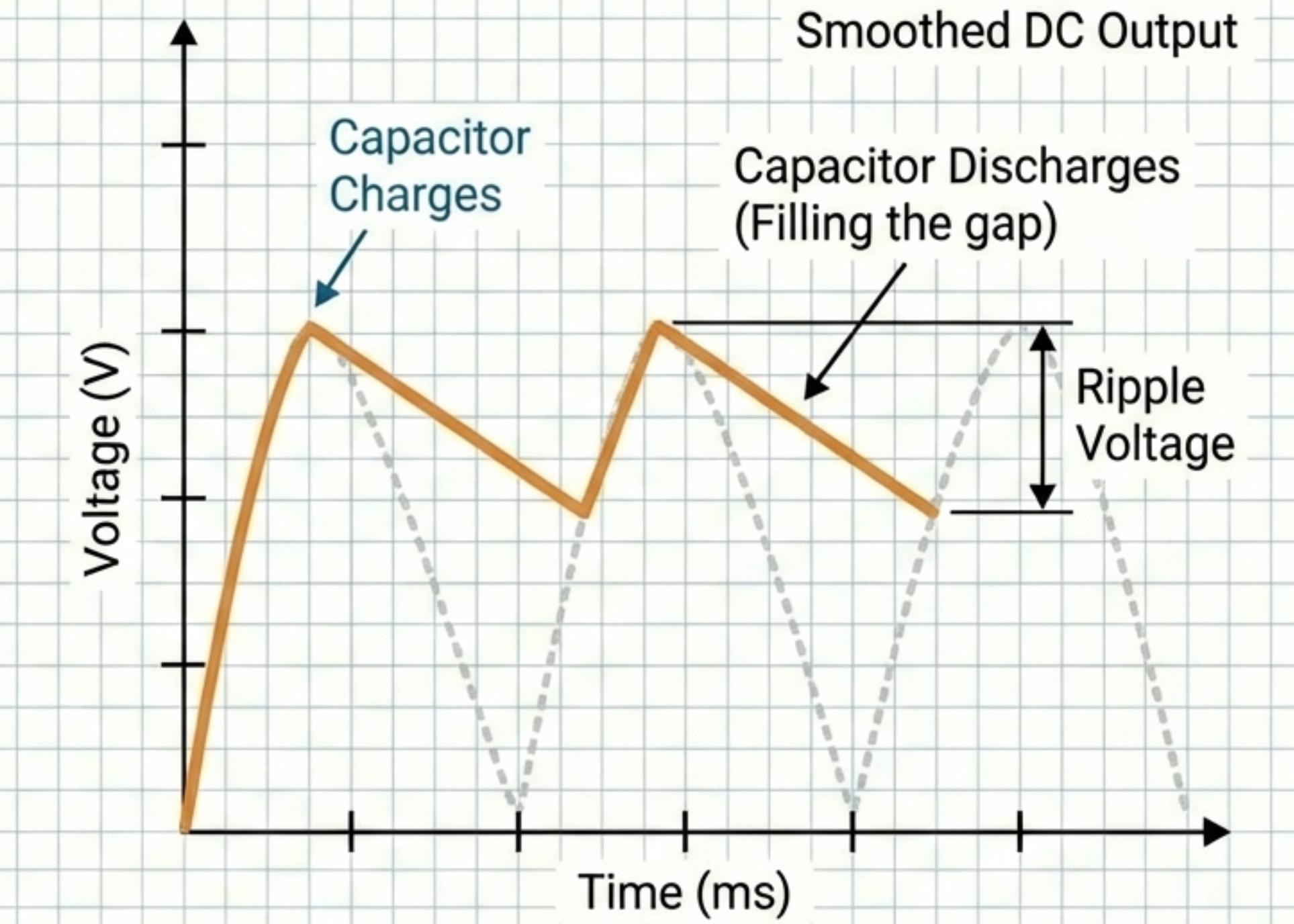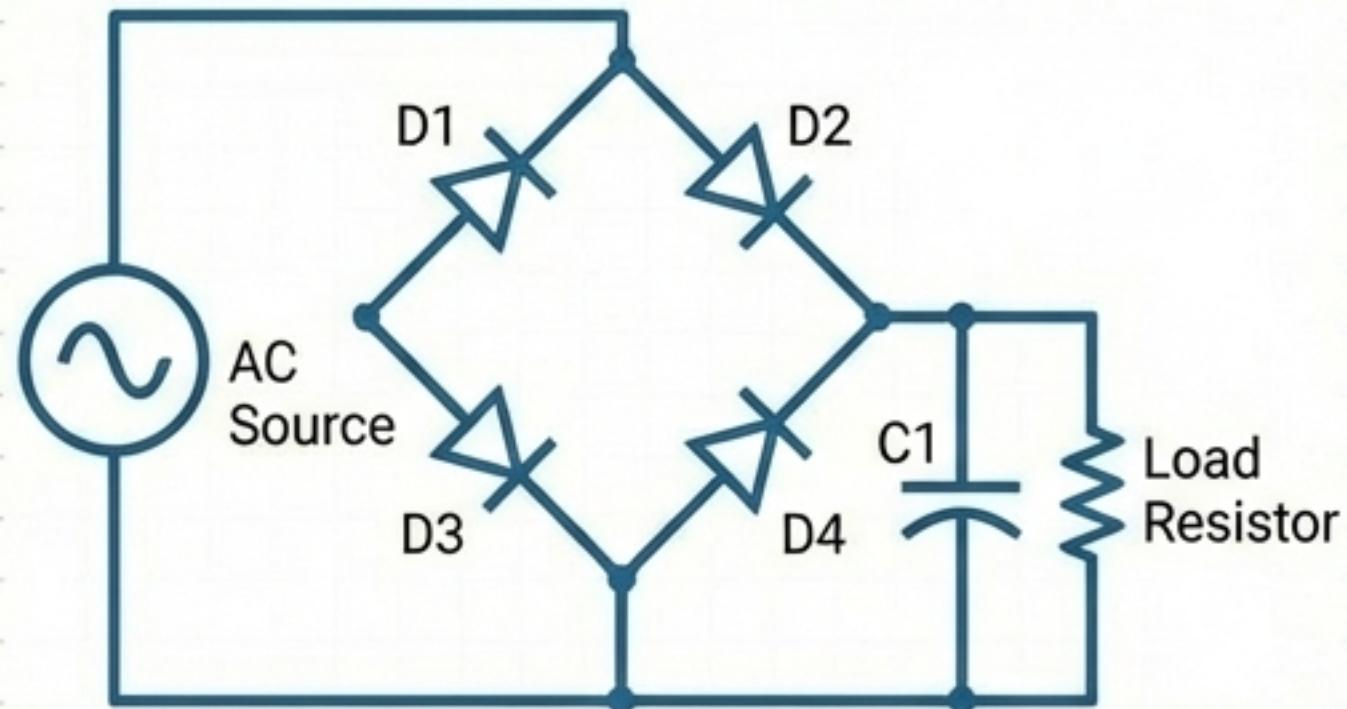


# Special Purpose Diodes

## Zener Diode




Voltage Regulation (Stabilization)

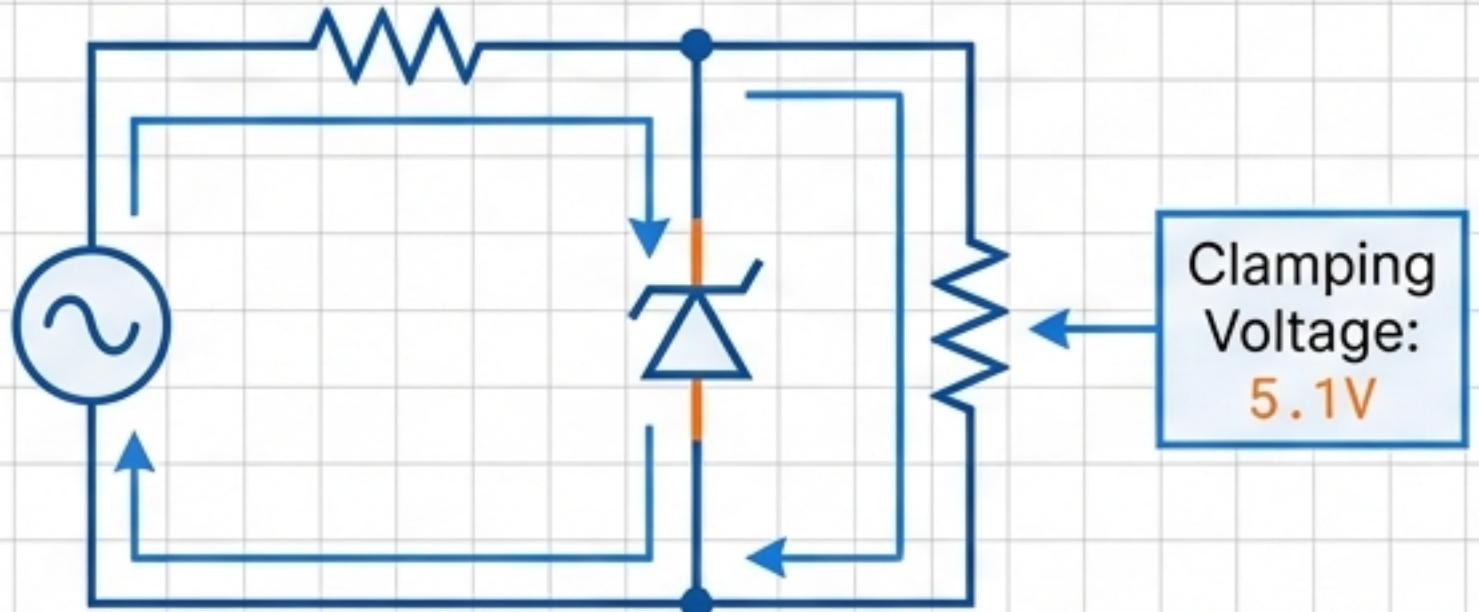


Operates in reverse breakdown to maintain constant voltage across load.

## LED (Light Emitting Diode)

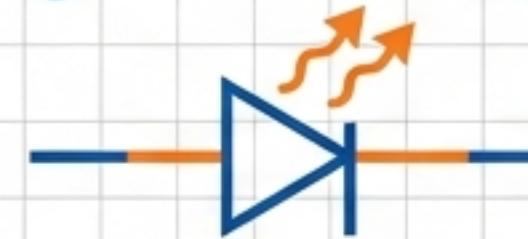

Long Leg: Anode (+) →

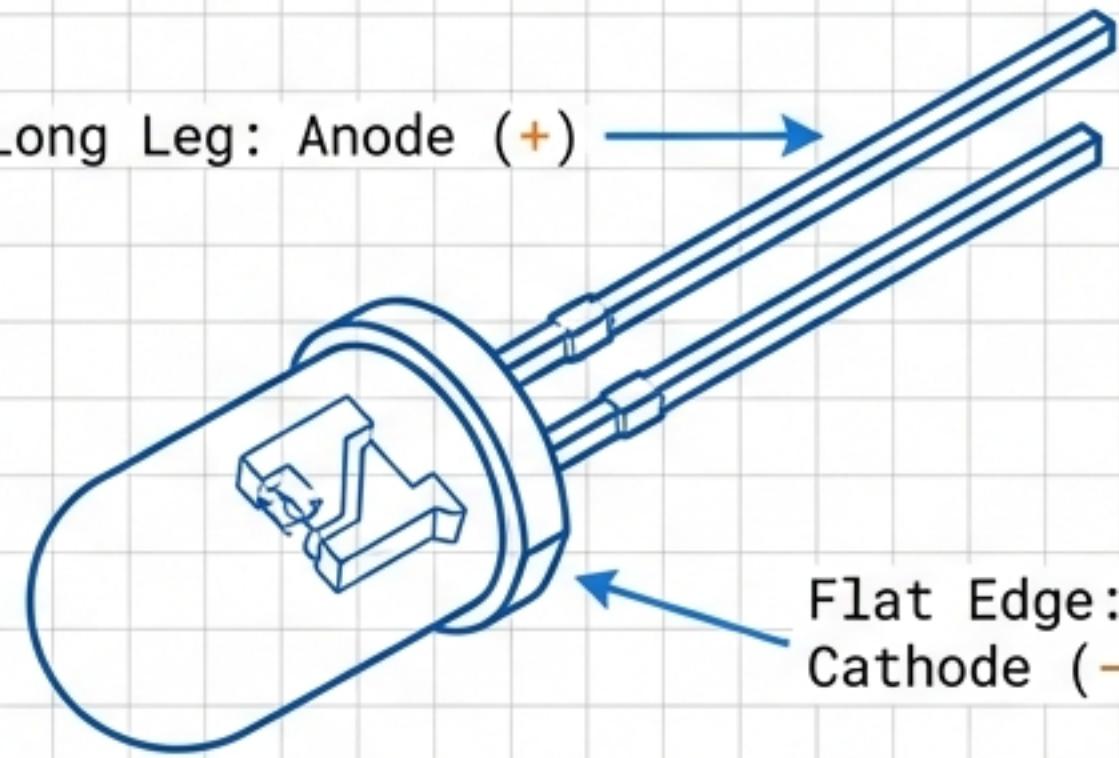

Flat Edge: Cathode (-)


**WARNING:** Must use Series Resistor to limit current.

Emits light when forward-biased; current must be limited to prevent burnout.

# Circuit Calculations: Ohm's Law

The Golden Rule: Subtract the Diode Drop (0.6V) First.

## Worked Example 2

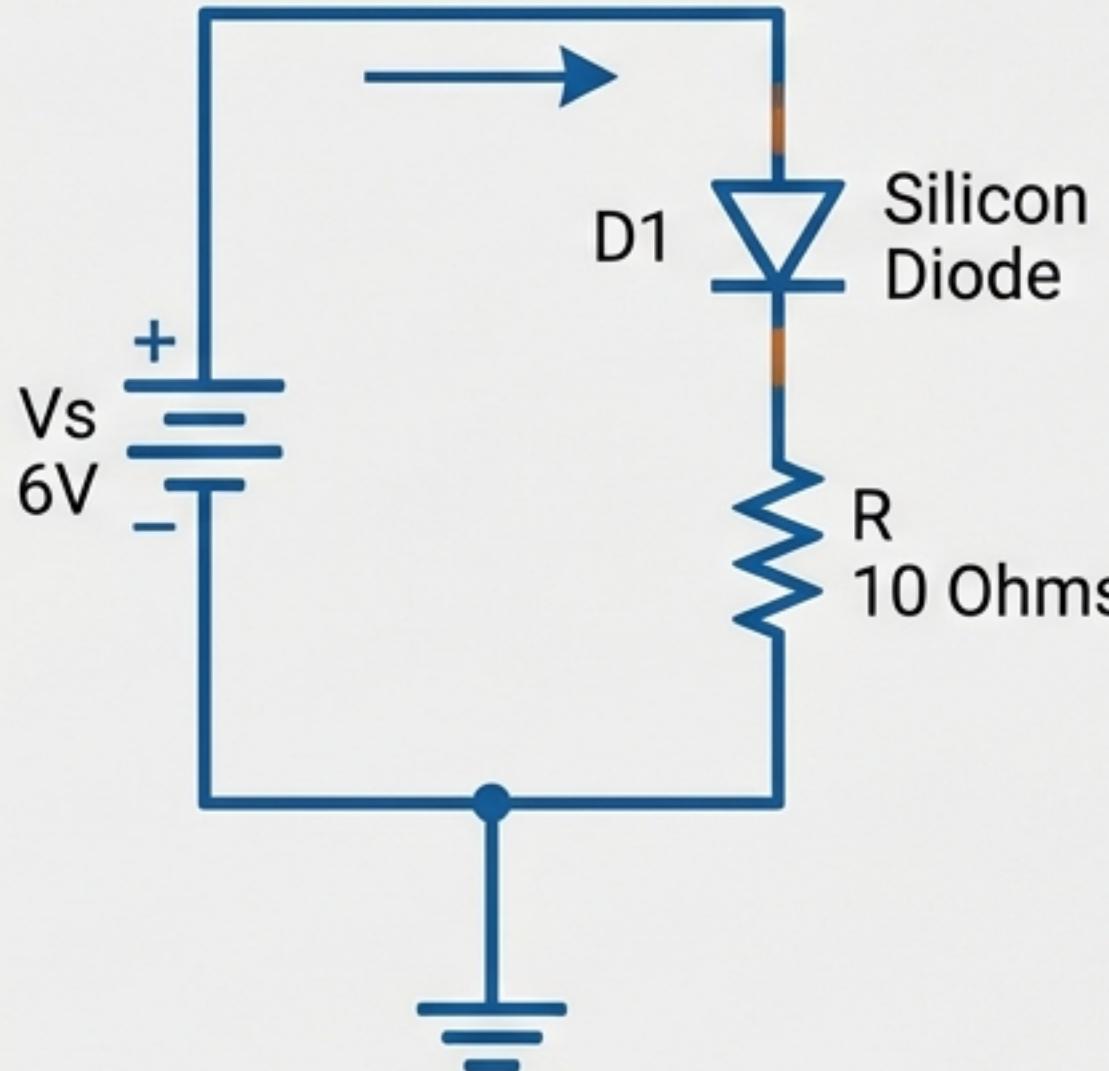

The Formula:

$$I = \frac{V_s - V_f}{R}$$

The Substitution:

$$I = \frac{6V - 0.6V}{10 \text{ Ohms}}$$

The Result:

$$I = \frac{5.4V}{10 \text{ Ohms}} = 0.54 \text{ A}$$





If Supply < 0.6V,  
Current = 0A.
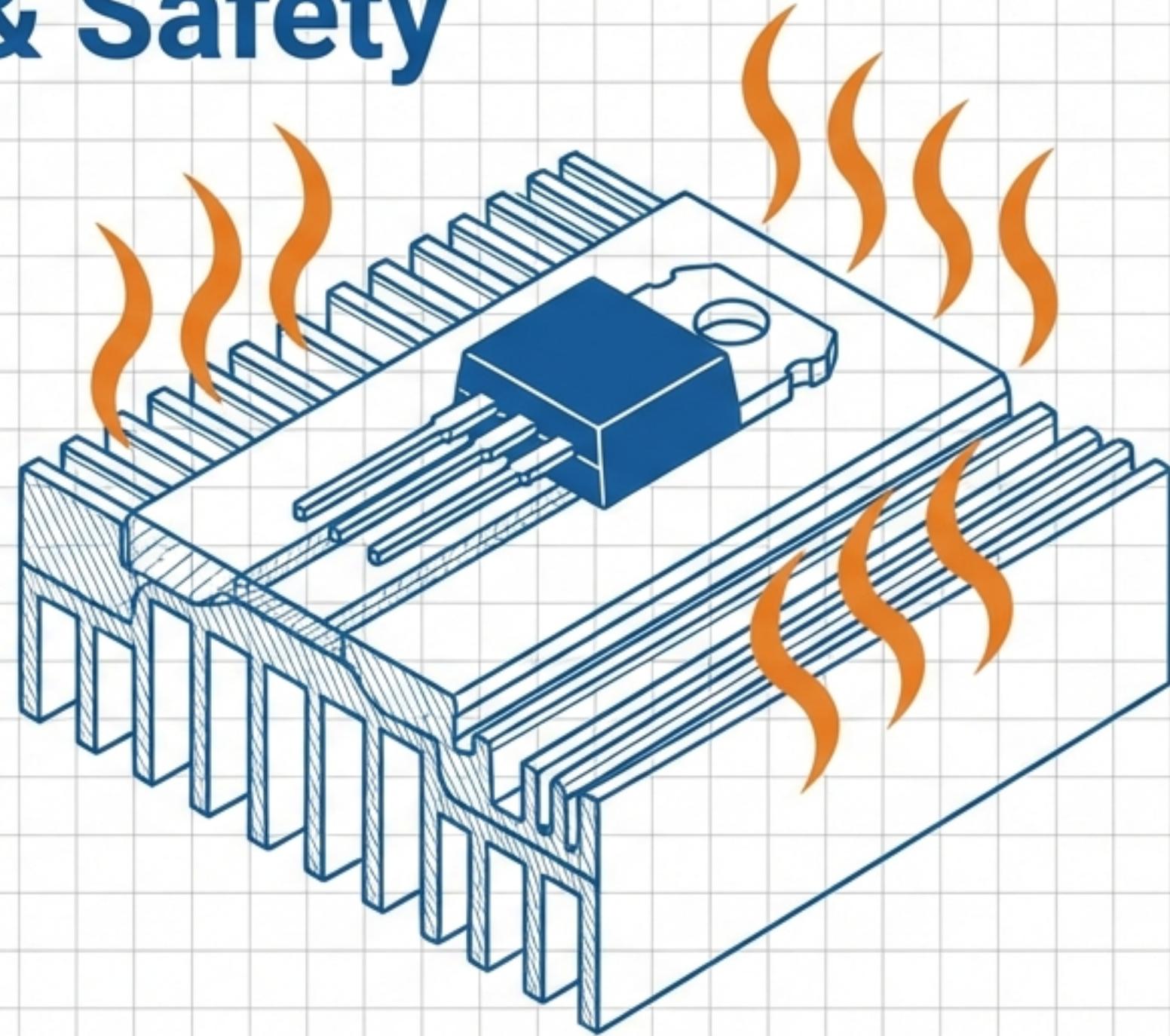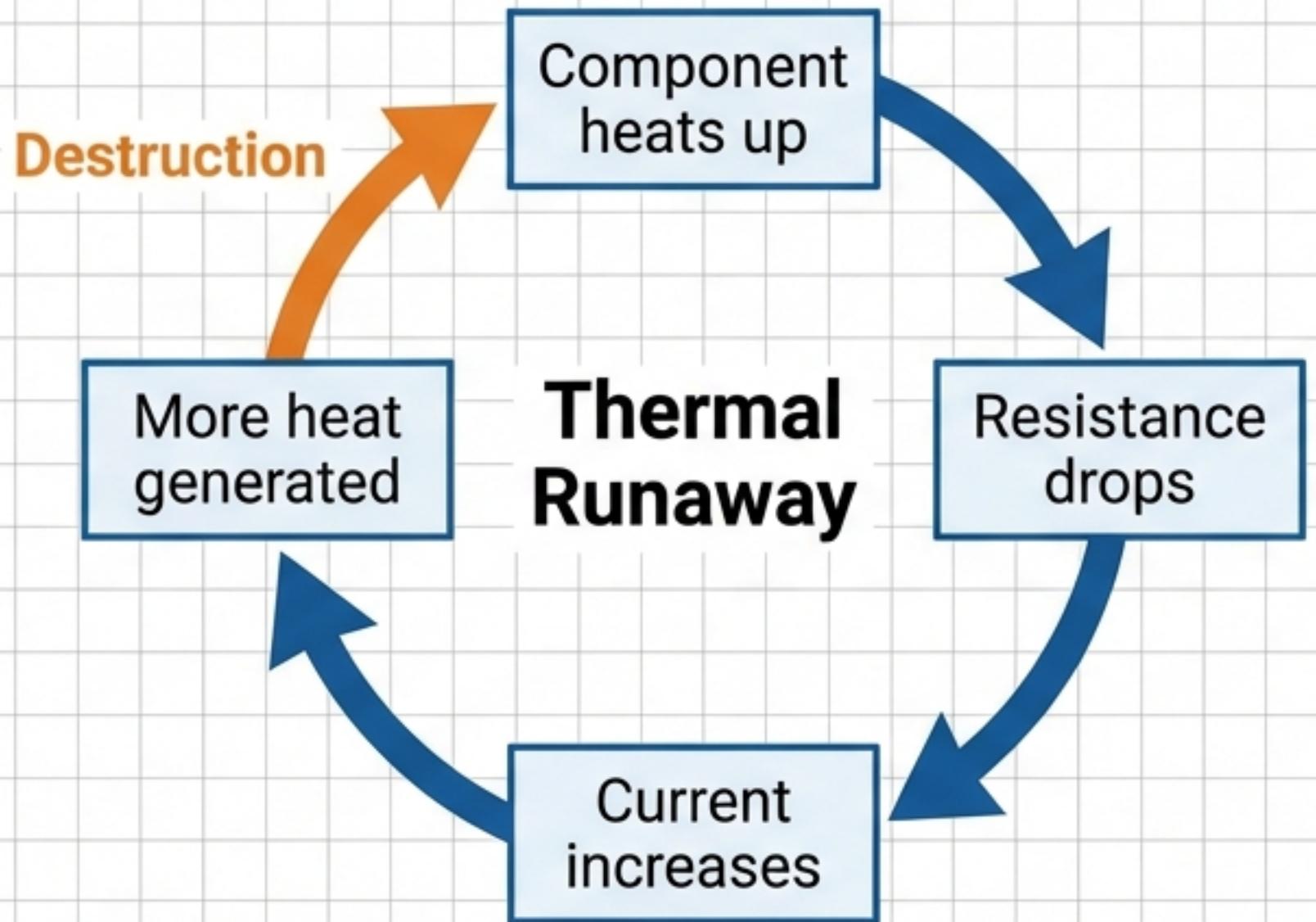
# Thermal Management & Safety

Power Loss (P)

$$= \text{Voltage Drop } (0.6V) \times \text{Current } (I)$$



Use Heat Sinks and Thermal Paste  
to dissipate energy.

# Unit 11 Essential Facts Cheat Sheet



## MATERIALS

Silicon (Si) = 4 Valence Electrons.  
**N-Type** = Pentavalent (Free Electrons).  
**P-Type** = Trivalent (Holes).



## THE BARRIER



Silicon Barrier Potential = **0.6V**.  
Germanium = **0.3V**.  
Must exceed this to conduct.



## RECTIFIERS



Half-Wave = 50Hz Ripple (Low Eff).  
Full-Wave = 100Hz Ripple (High Eff).



## SAFETY



Always **subtract 0.6V** before calc.  
Always use resistor with LED.  
**Zener** used for Voltage Reg.

End of Unit 11.